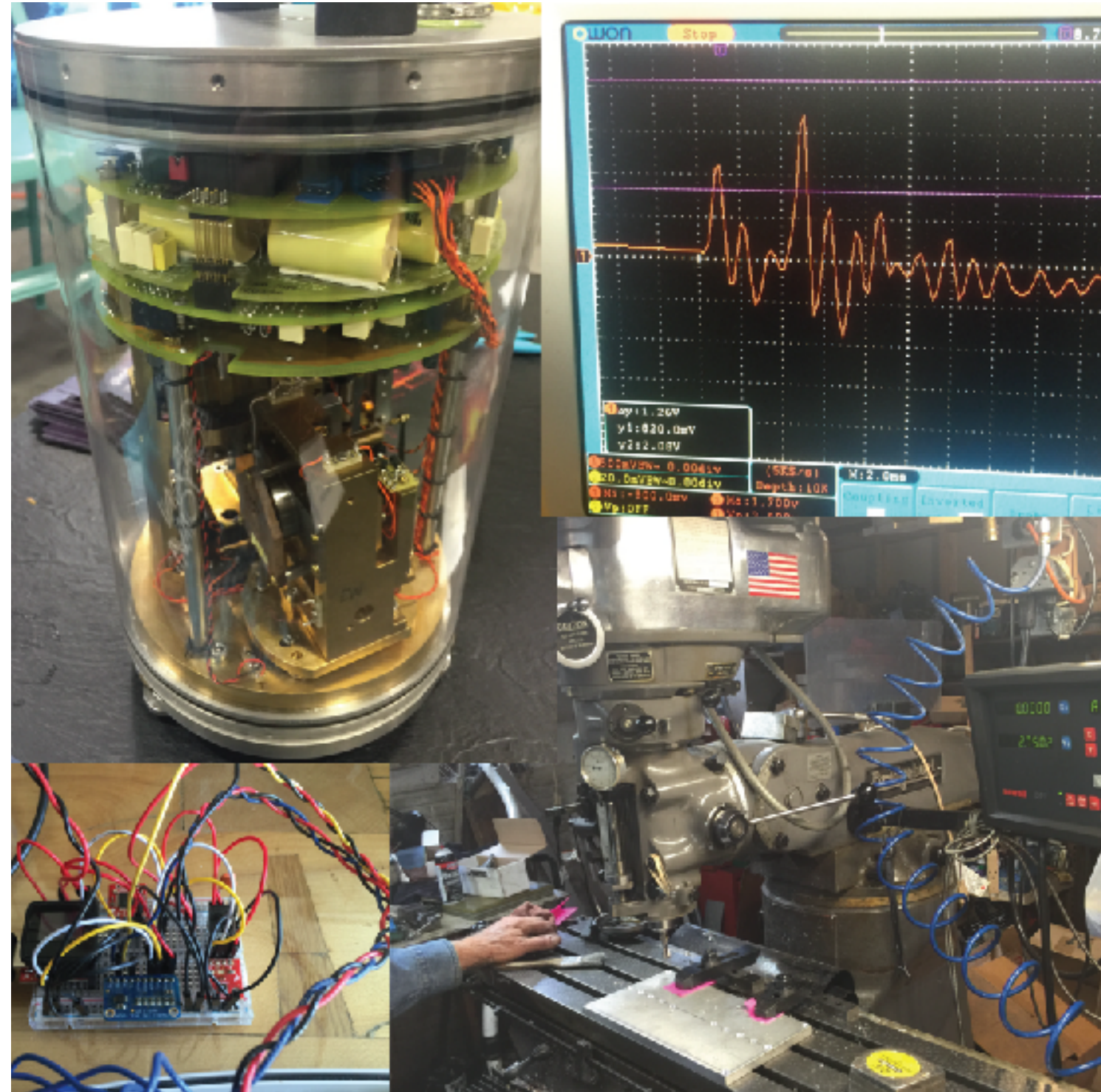


# Operational Amplifiers - Part 1

J.R. Leeman and C. Marone

Techniques of Geoscientific  
Experimentation

October 27, 2016





**In the lab, operational amplifiers are often used to make small signals larger so we can more easily measure them**



**In the lab, operational amplifiers are often used to make small signals larger so we can more easily measure them**

$$\frac{124.06 \text{ mV} - 123.47 \text{ mV}}{10 \text{ lbs} - 0 \text{ lbs}} = 0.059 \text{ mV/lb} \text{ or } 0.000059 \text{ V/lb}$$

**In the lab, operational amplifiers are often used to make small signals larger so we can more easily measure them**

$$\frac{124.06 \text{ mV} - 123.47 \text{ mV}}{10 \text{ lbs} - 0 \text{ lbs}} = 0.059 \text{ mV/lb} \text{ or } 0.000059 \text{ V/lb}$$

**X1000!**

**In the lab, operational amplifiers are often used to make small signals larger so we can more easily measure them**


$$\frac{124.06 \text{ mV} - 123.47 \text{ mV}}{10 \text{ lbs} - 0 \text{ lbs}} = 0.059 \text{ mV/lb} \text{ or } 0.000059 \text{ V/lb}$$

**X1000!**


$$= 590 \text{ mV/lb} \text{ or } 0.59 \text{ V/lb}$$



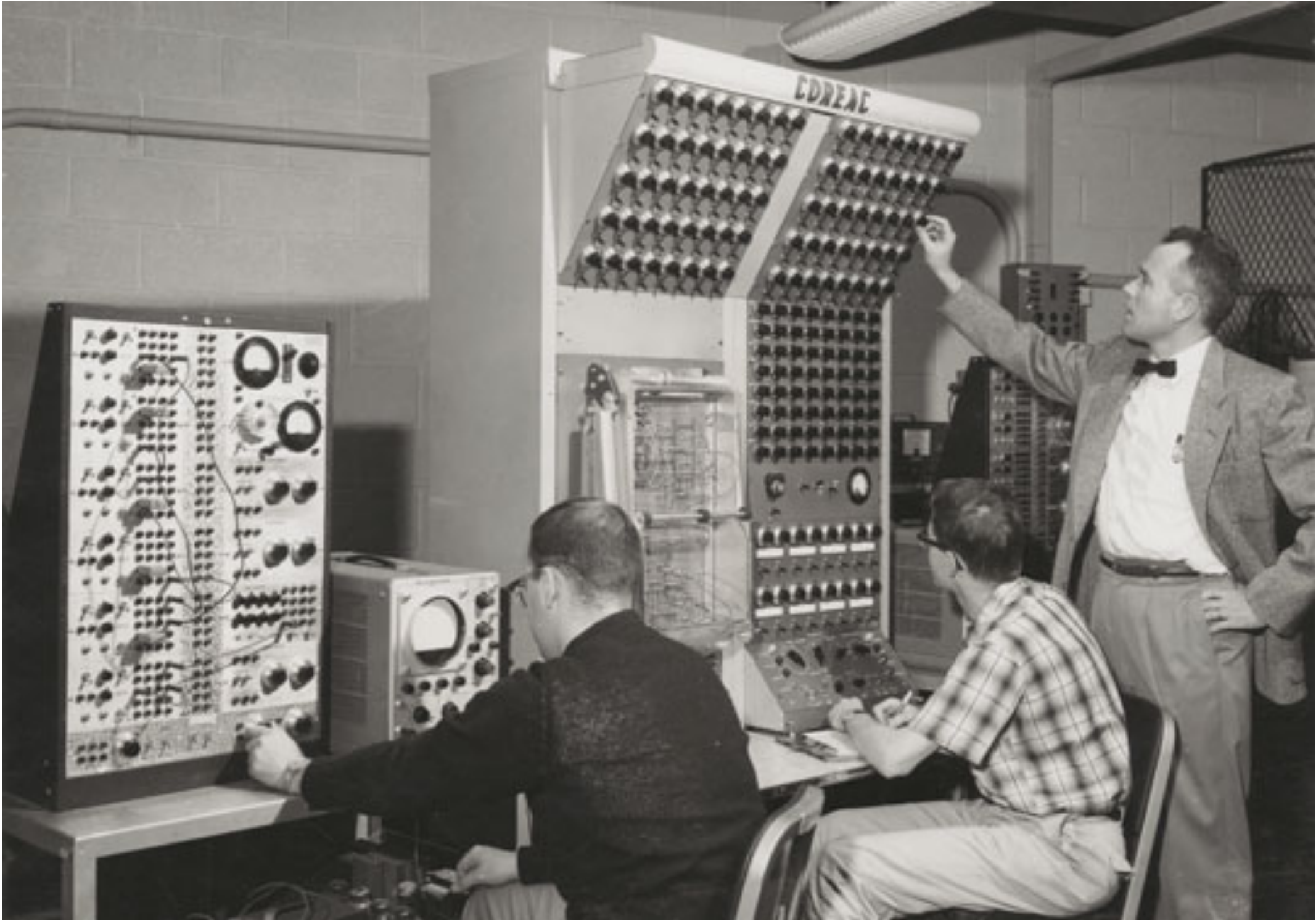
# The name operational amplifiers implies more than a simple amplifier though


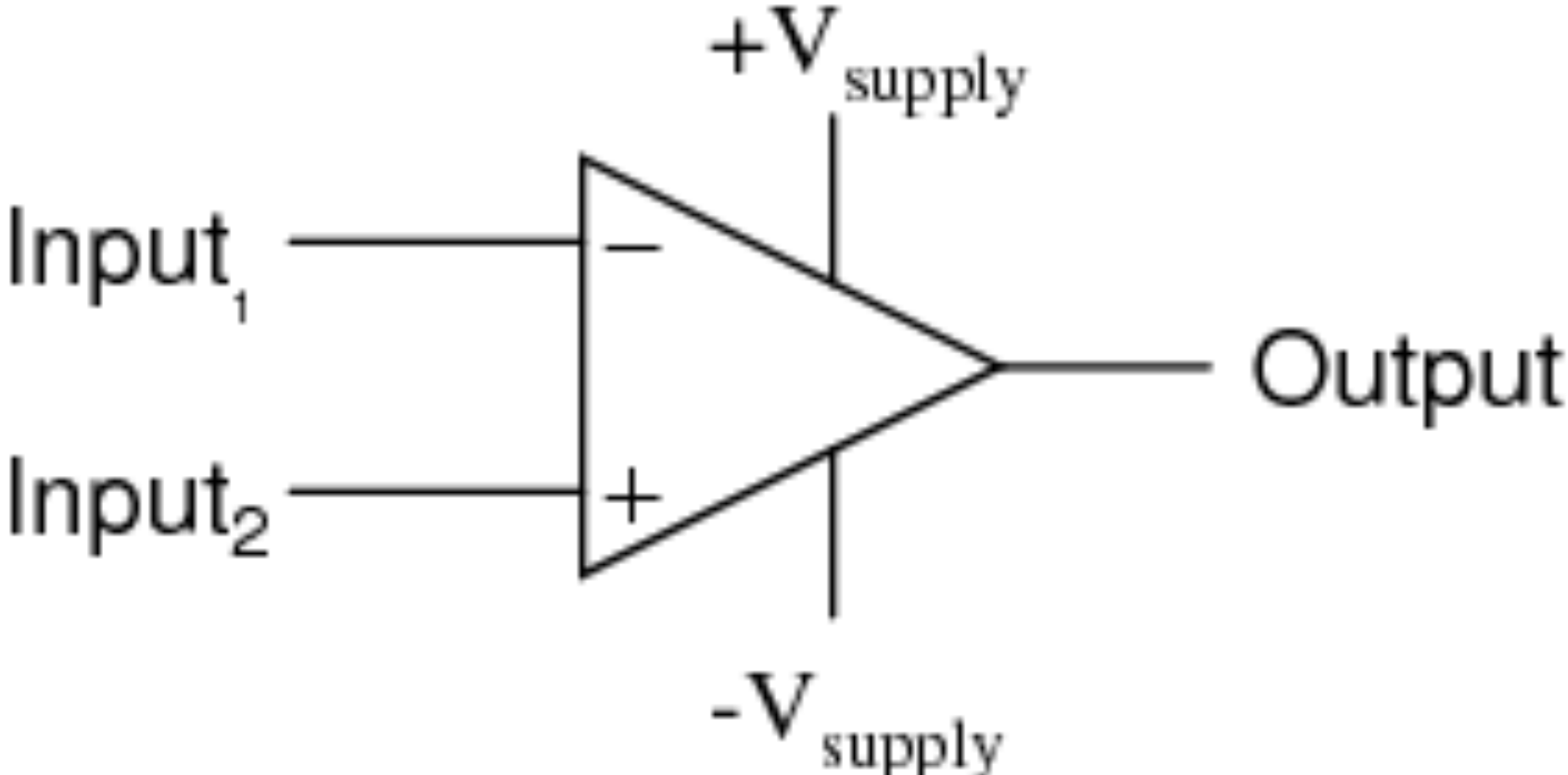
# Let's look at some terminals of the operational amplifier



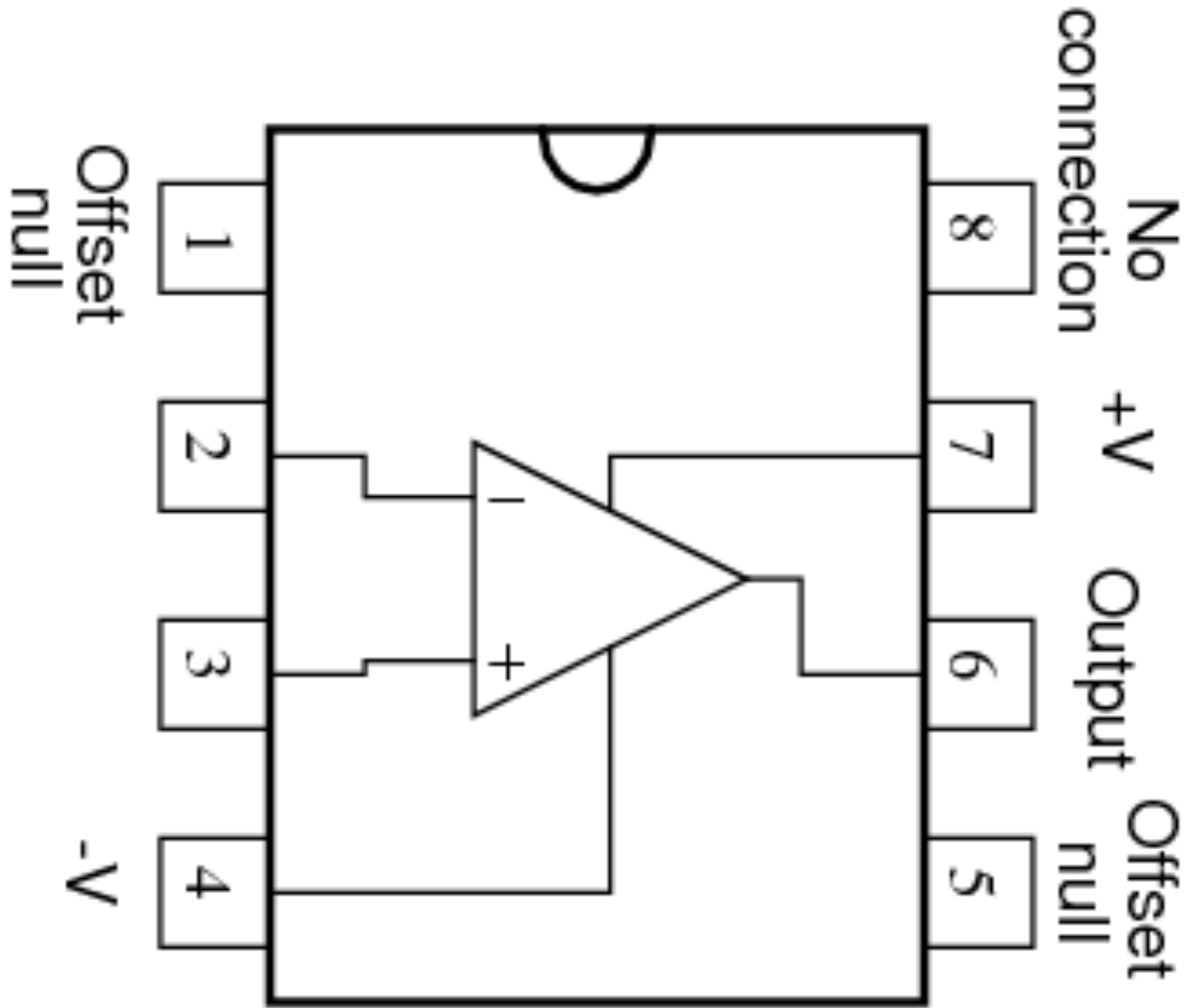Real amplifiers have a few more connections that we'll get to








# Understanding the ideal op-amp is enough to examine many circuits, but can be problematic in actual design

1. Infinite open-loop voltage gain
2. Infinite input impedance
3. Zero output impedance
4. Zero noise contribution
5. Zero DC output offset
6. Infinite bandwidth
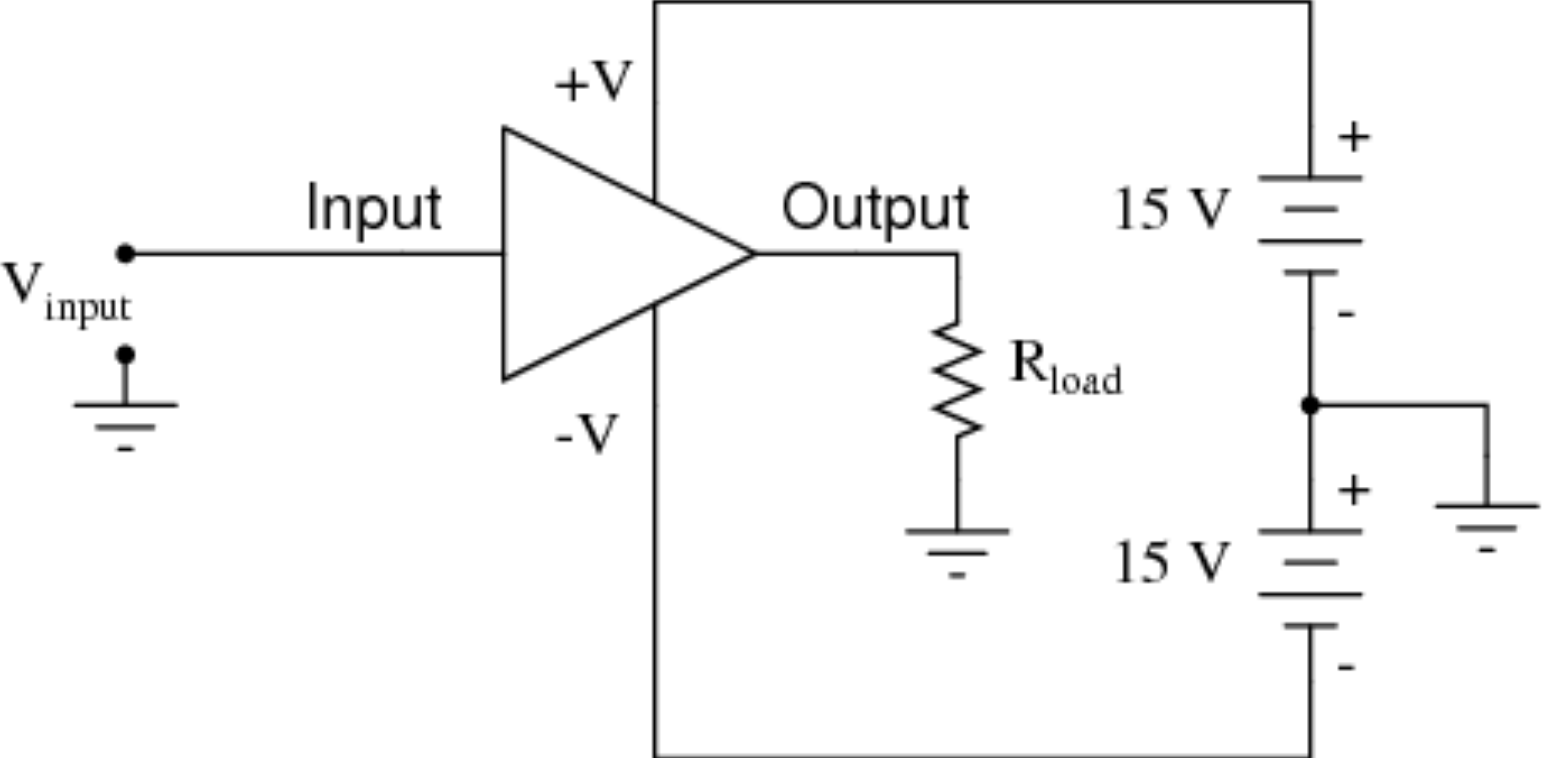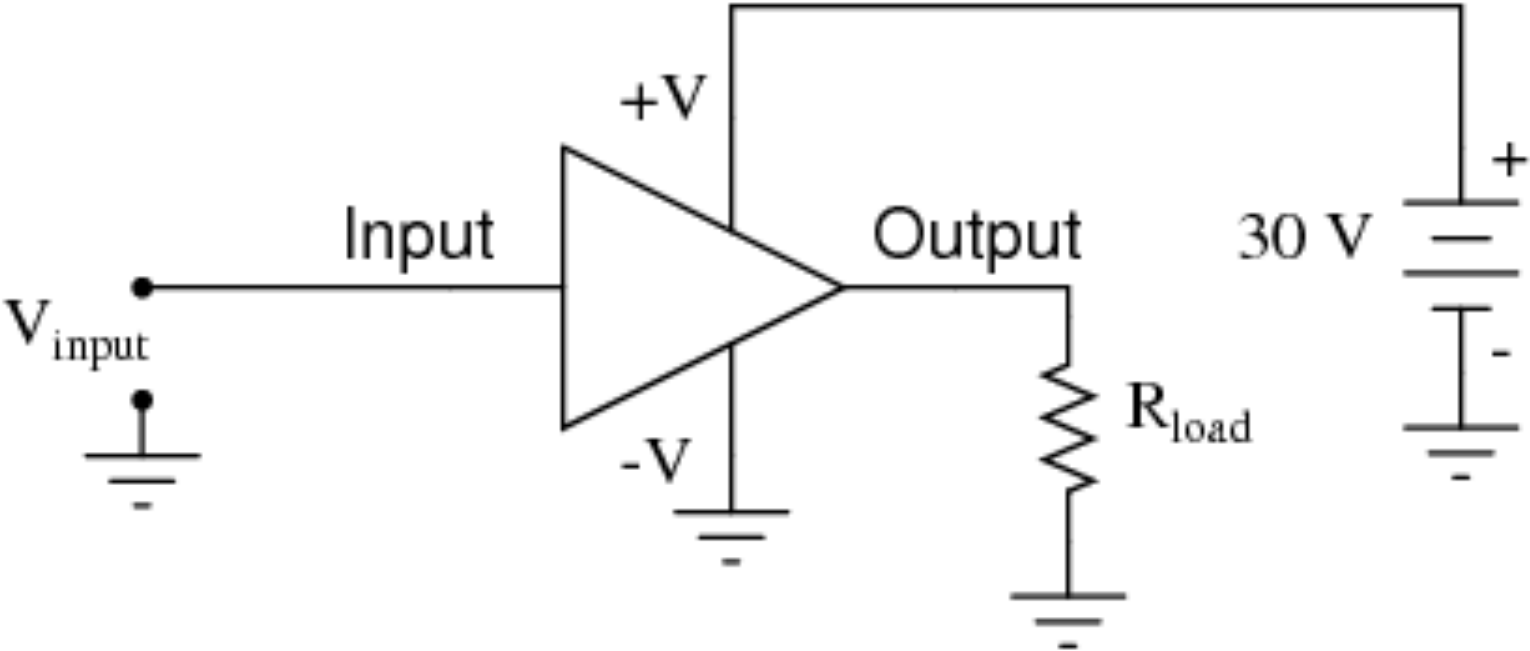
# Op-amps can be powered by unipolar or bipolar power supplies



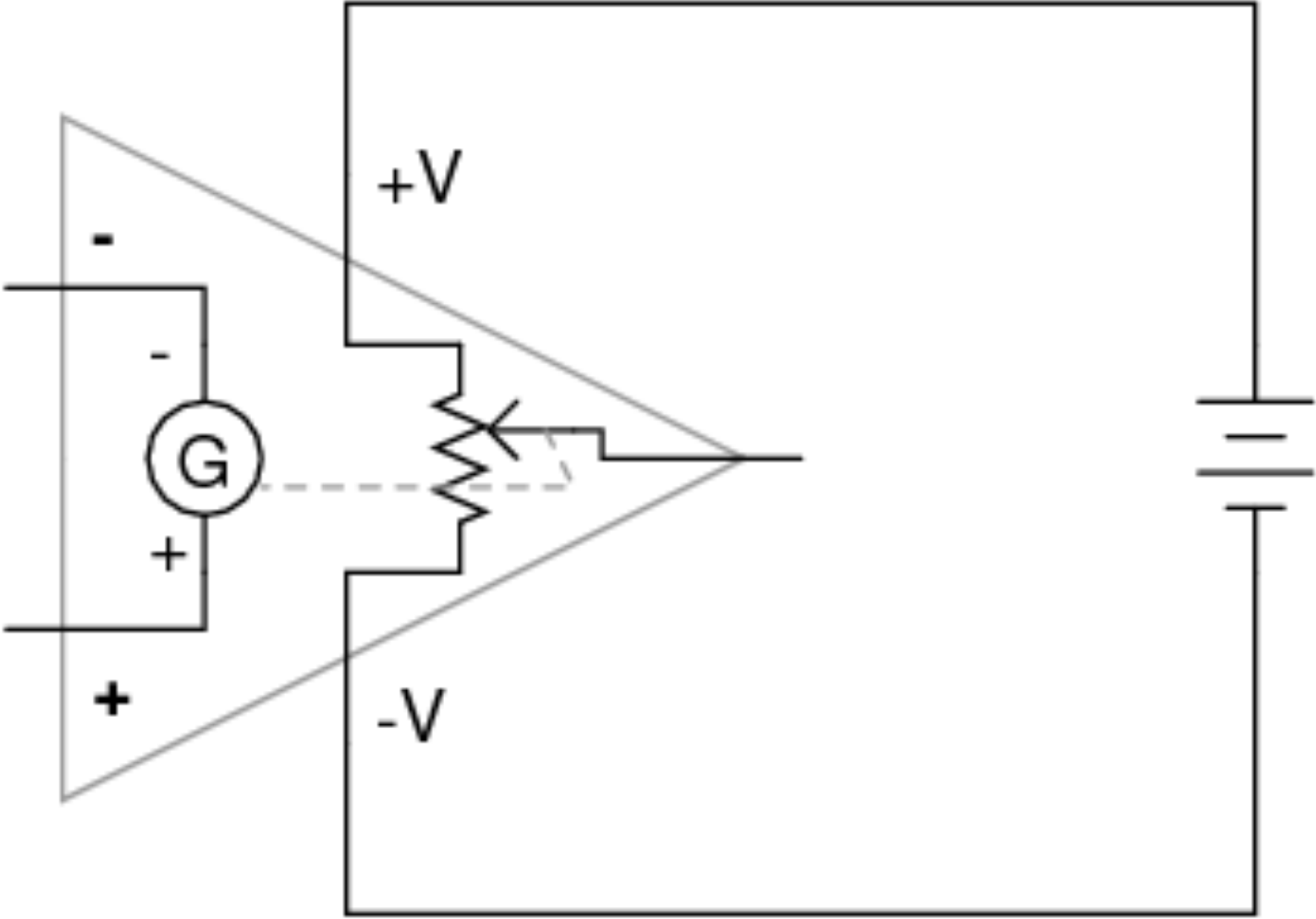**You can think of an operational amplifier in this simplified model - the output should always be the sum of the inputs with the open loop gain applied!**



Open loop gain is the gain with NO feedback from output to input.  
It is generally 20,000 - 200,000 in real op-amps


## LM741 Operational Amplifier

### 6.5 Electrical Characteristics, LM741<sup>(1)</sup>



PARAMETER	TEST CONDITIONS	MIN	TYP	MAX	UNIT
Input offset voltage	$R_S \leq 10 \text{ k}\Omega$	$T_A = 25^\circ\text{C}$	1	5	mV
		$T_{AMIN} \leq T_A \leq T_{AMAX}$		6	mV
Input offset voltage adjustment range	$T_A = 25^\circ\text{C}, V_S = \pm 20 \text{ V}$		$\pm 15$		mV
Input offset current	$T_A = 25^\circ\text{C}$ $T_{AMIN} \leq T_A \leq T_{AMAX}$		20	200	nA
			85	500	
Input bias current	$T_A = 25^\circ\text{C}$ $T_{AMIN} \leq T_A \leq T_{AMAX}$		80	500	nA
				1.5	$\mu\text{A}$
Input resistance	$T_A = 25^\circ\text{C}, V_S = \pm 20 \text{ V}$	0.3	2		M $\Omega$
Input voltage range	$T_{AMIN} \leq T_A \leq T_{AMAX}$	$\pm 12$	$\pm 13$		V
Large signal voltage gain	$V_S = \pm 15 \text{ V}, V_O = \pm 10 \text{ V}, R_L \geq 2 \text{ k}\Omega$	$T_A = 25^\circ\text{C}$	50	200	V/mV
		$T_{AMIN} \leq T_A \leq T_{AMAX}$	25		
Output voltage swing	$V_S = \pm 15 \text{ V}$	$R_L \geq 10 \text{ k}\Omega$	$\pm 12$	$\pm 14$	V
		$R_L \geq 2 \text{ k}\Omega$	$\pm 10$	$\pm 13$	
Output short circuit current	$T_A = 25^\circ\text{C}$		25		mA
Common-mode rejection ratio	$R_S \leq 10 \Omega, V_{CM} = \pm 12 \text{ V}, T_{AMIN} \leq T_A \leq T_{AMAX}$	80	95		dB
Supply voltage rejection ratio	$V_S = \pm 20 \text{ V to } \pm 5 \text{ V}, R_S \leq 10 \Omega, T_{AMIN} \leq T_A \leq T_{AMAX}$	86	96		dB
Transient response	Rise time	$T_A = 25^\circ\text{C}, \text{ unity gain}$		0.3	$\mu\text{s}$
			Overshoot		
Slew rate	$T_A = 25^\circ\text{C}, \text{ unity gain}$		0.5		V/ $\mu\text{s}$
Supply current	$T_A = 25^\circ\text{C}$		1.7	2.8	mA
Power consumption	$V_S = \pm 15 \text{ V}$	$T_A = 25^\circ\text{C}$	50	85	mW
		$T_A = T_{AMIN}$	60	100	
		$T_A = T_{AMAX}$	45	75	



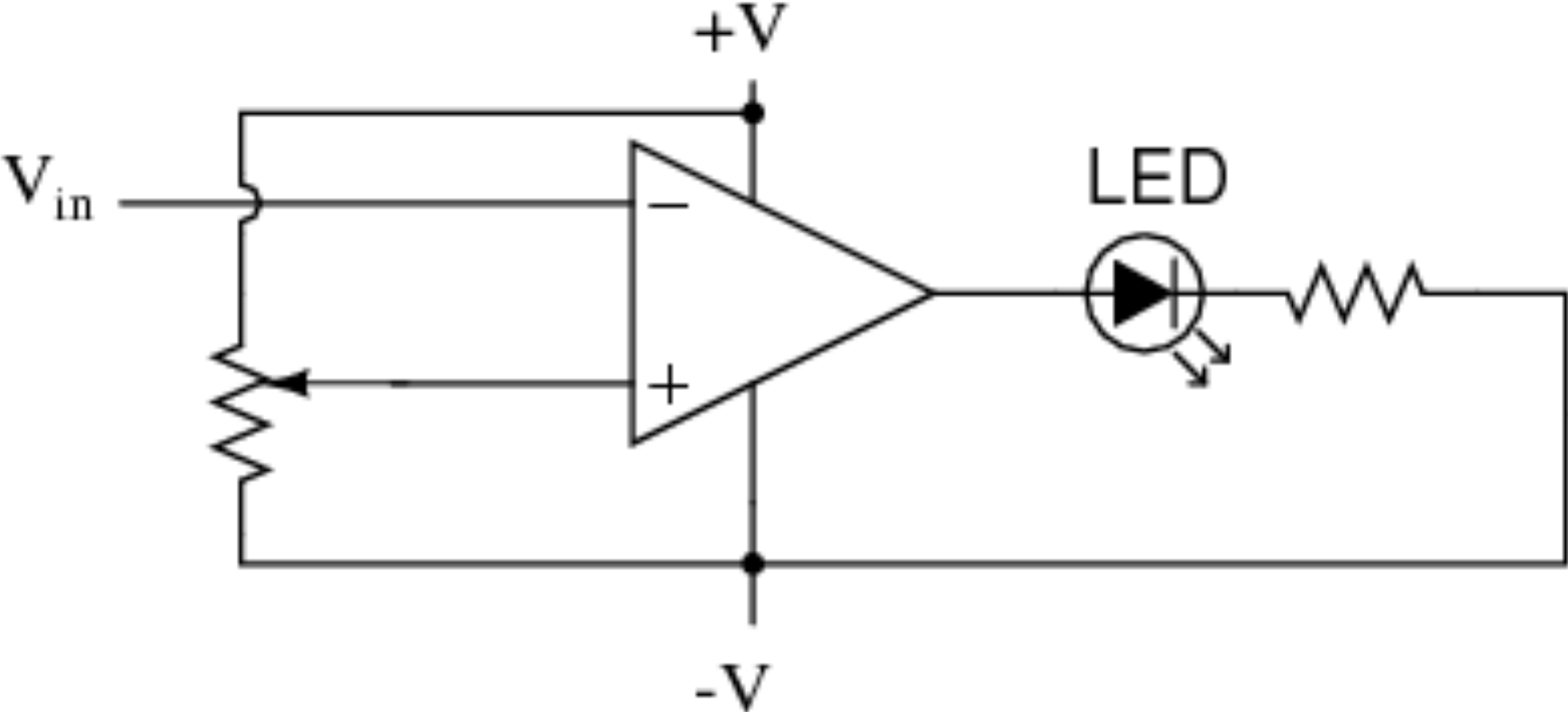
In an open loop configuration we can build a voltage comparator



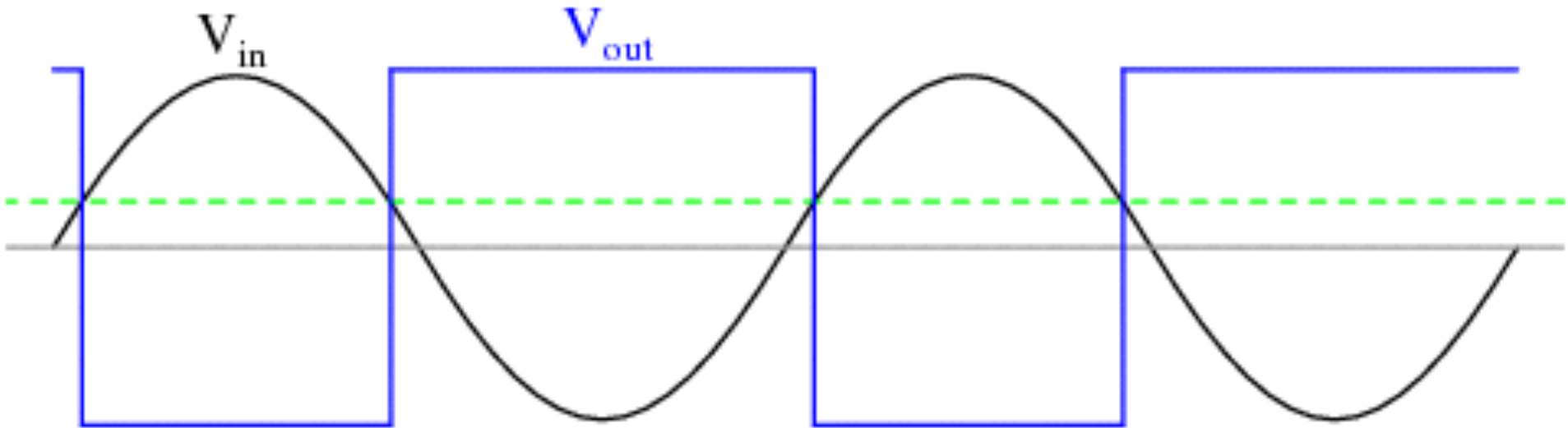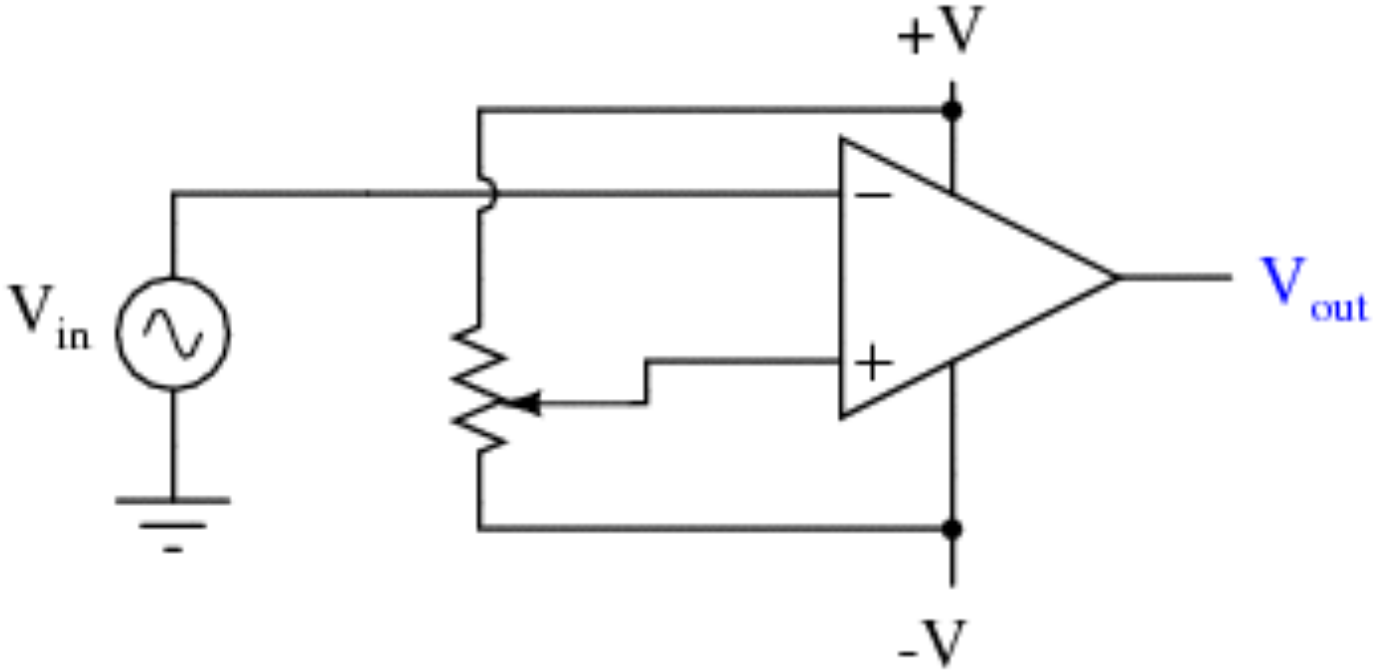
# Squaring up a waveform is another common application


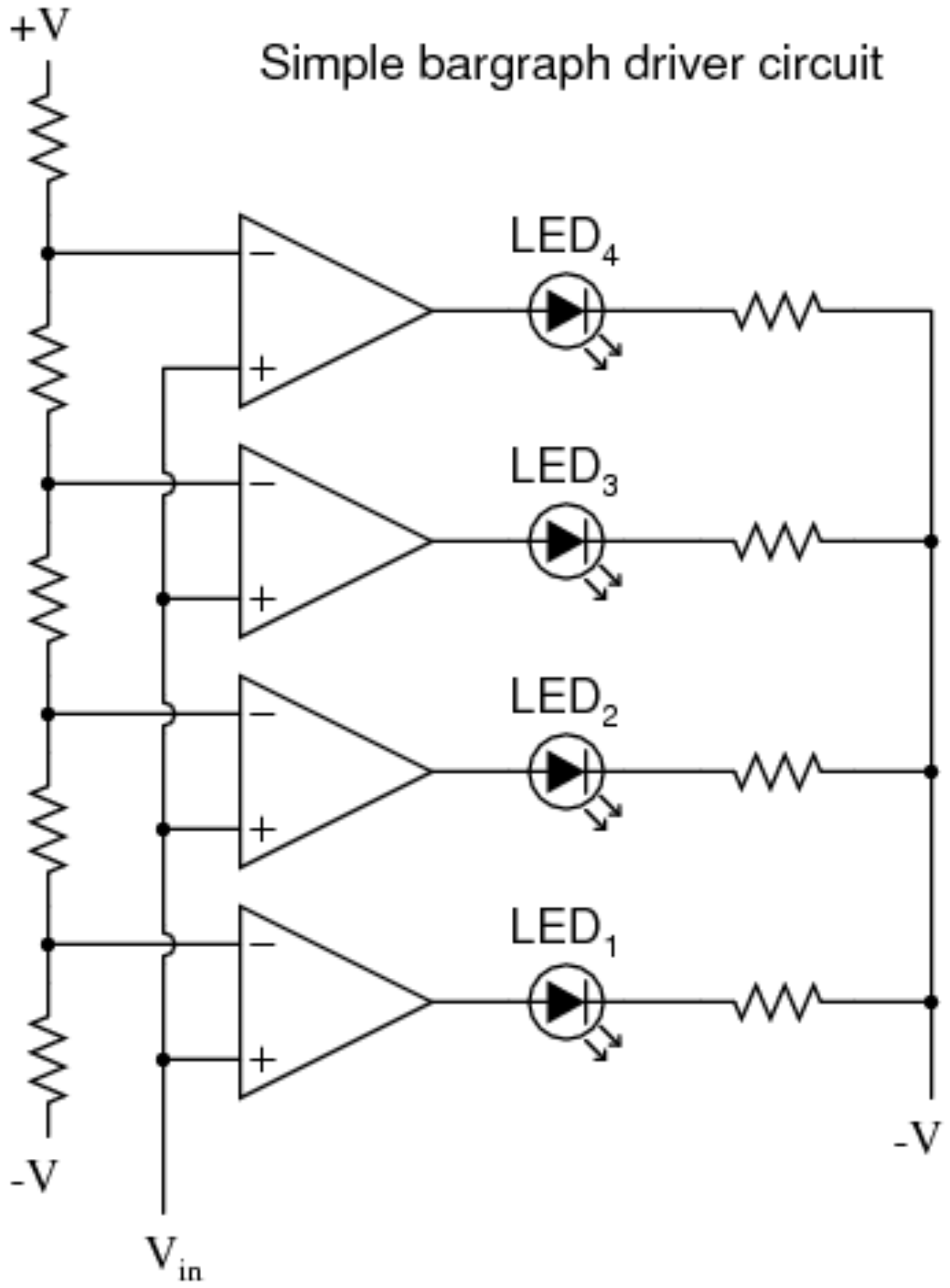
# A voltage divider and series of comparators can make an LED bargraph driver



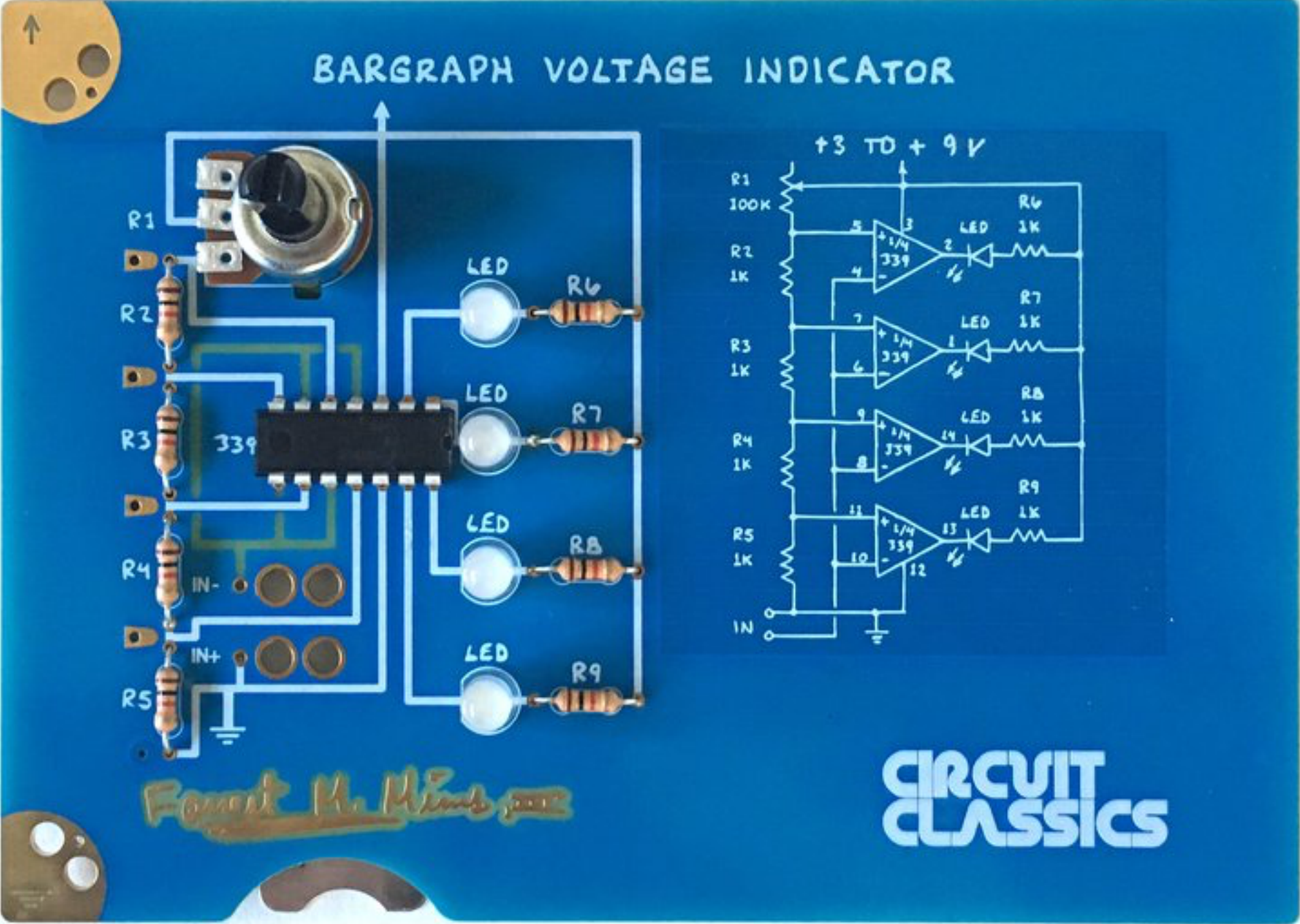
# A voltage divider and series of comparators can make an LED bargraph driver






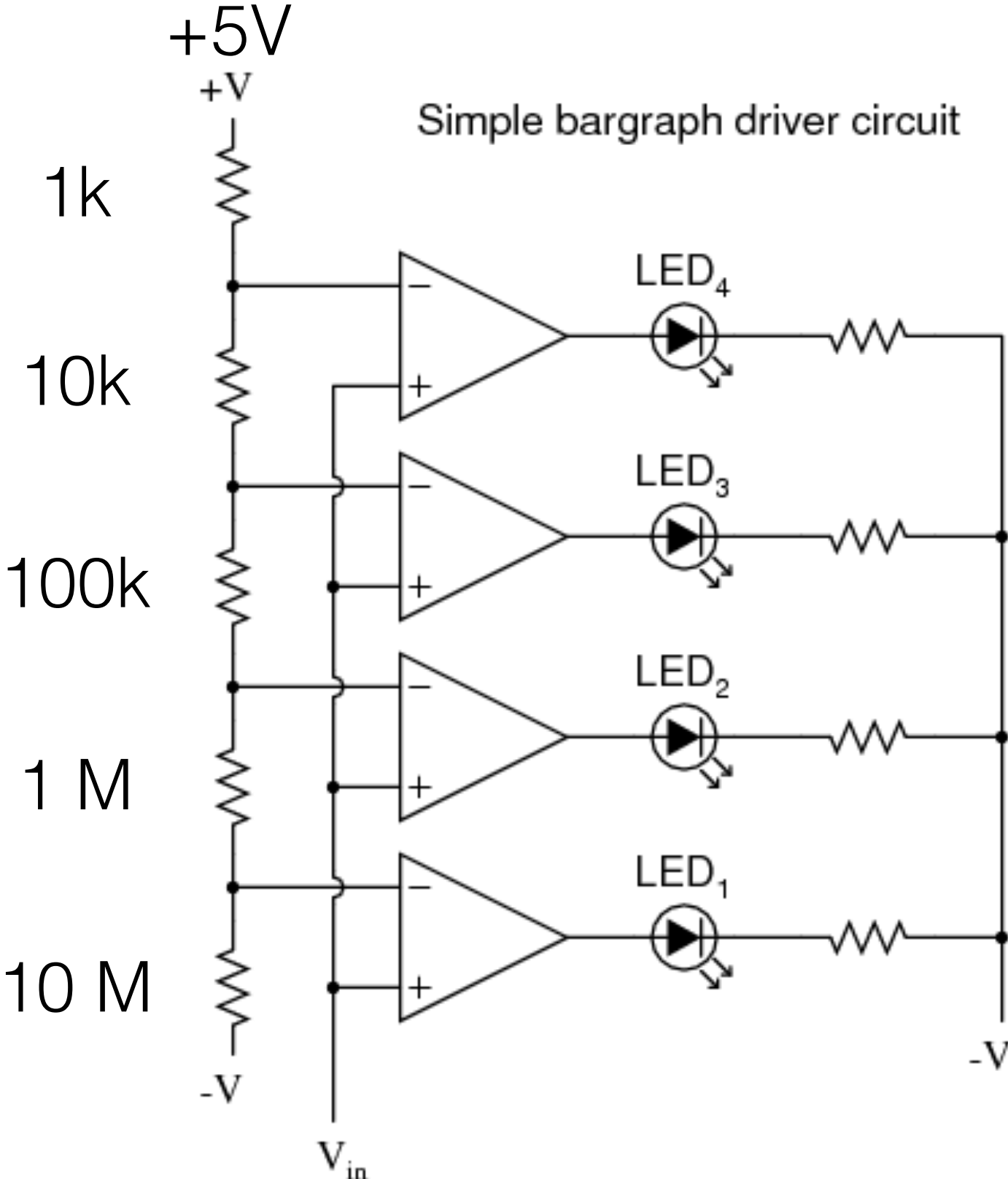
# Activity: Calculate the voltage at which each LED will switch on



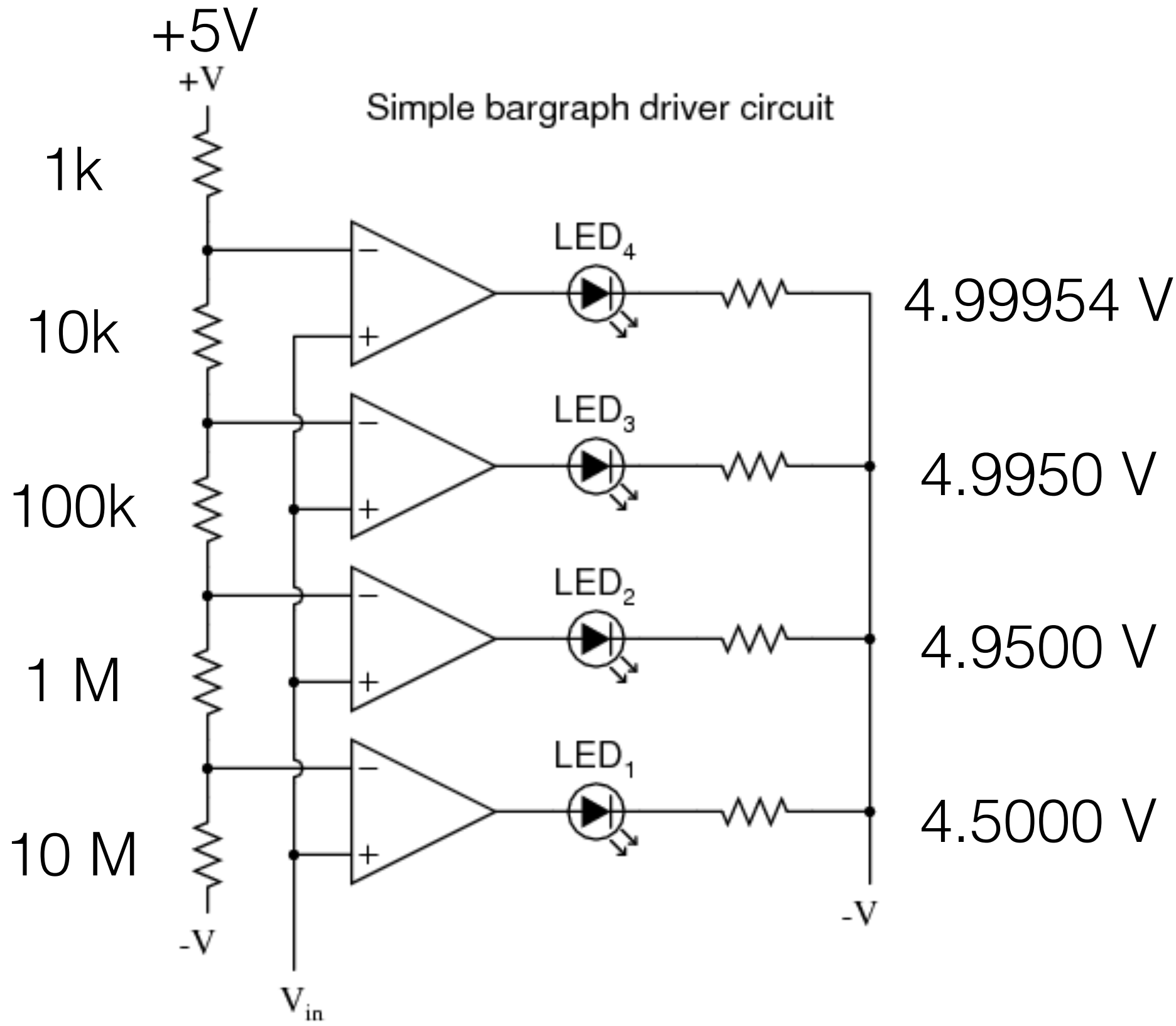
# Activity: Calculate the voltage at which each LED will switch on



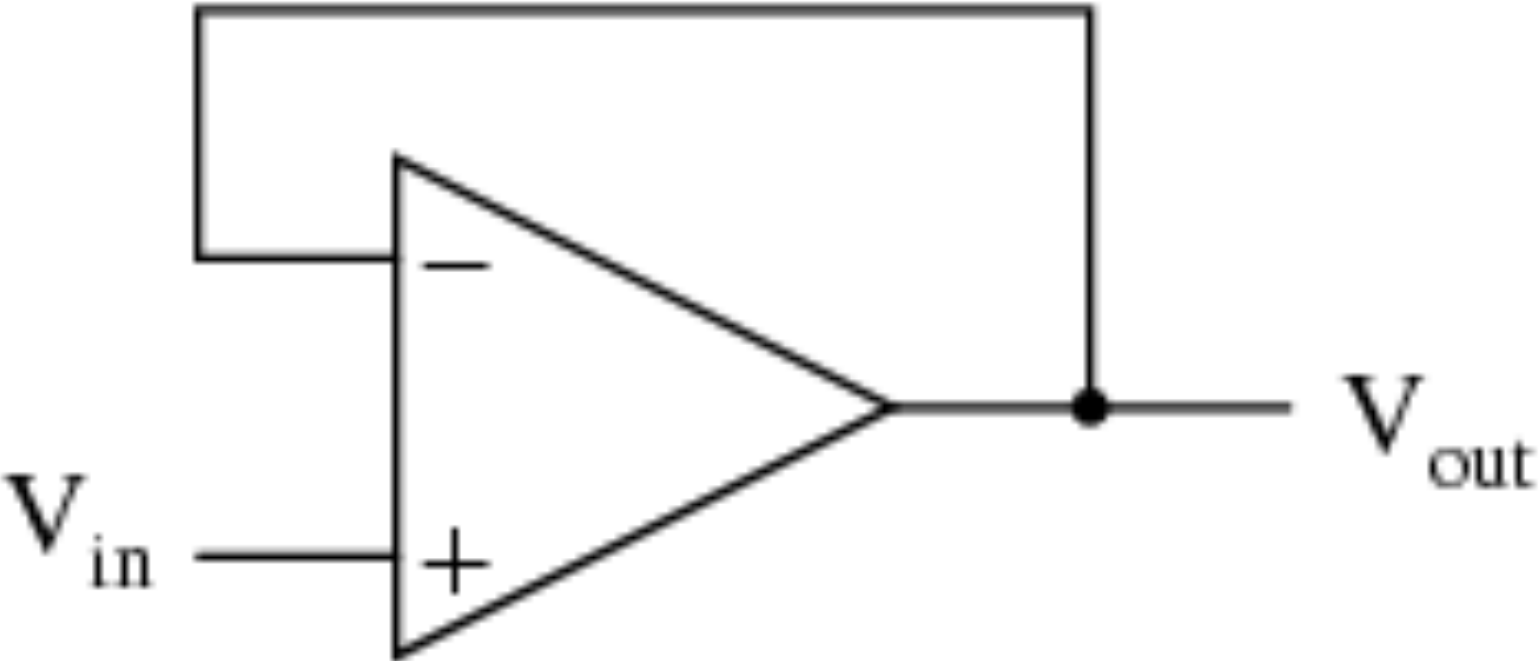**What happens if we hook up the amplifier with negative feedback?**




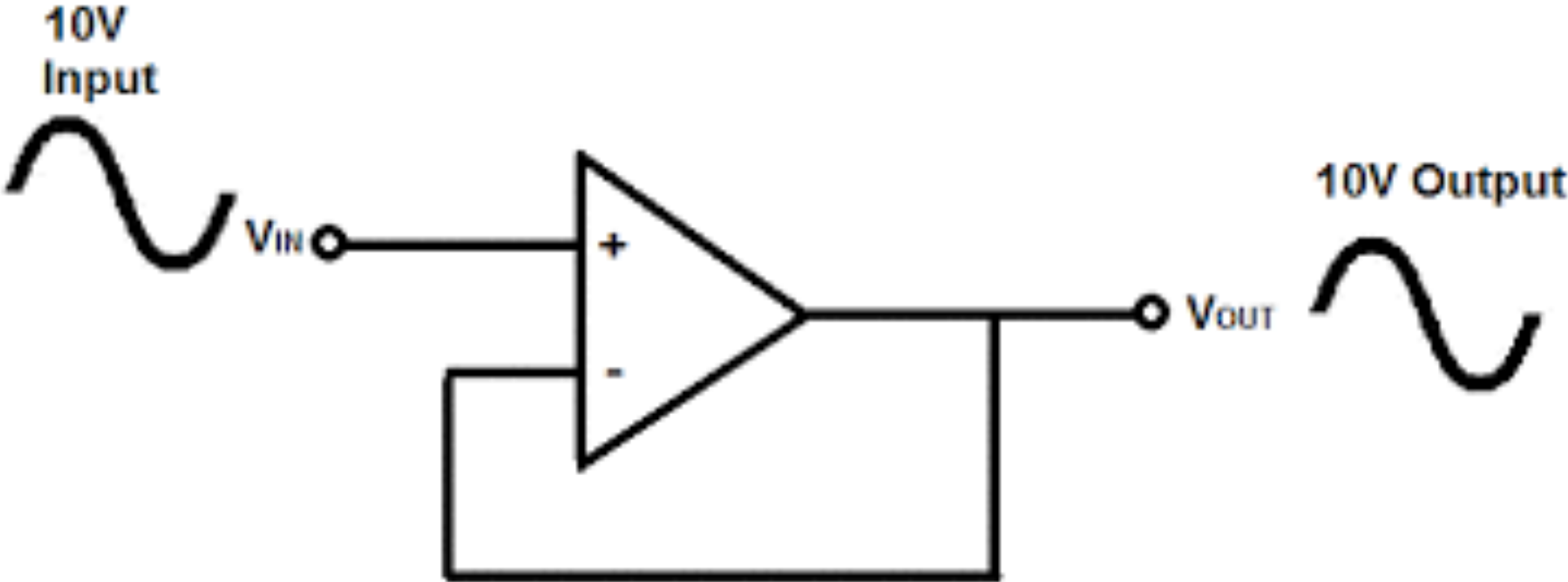This circuit is called a voltage follower






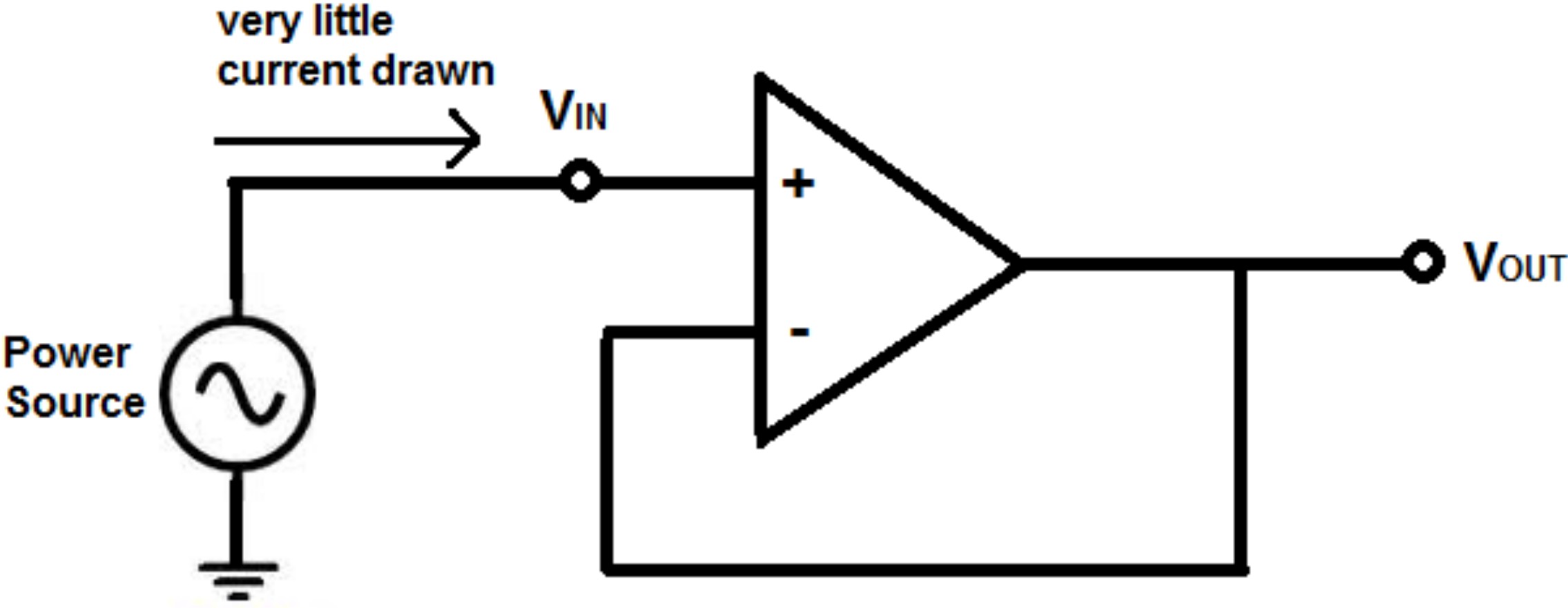We use voltage followers to buffer between our signal and the load (think back to the ideal op-amp “rules”)



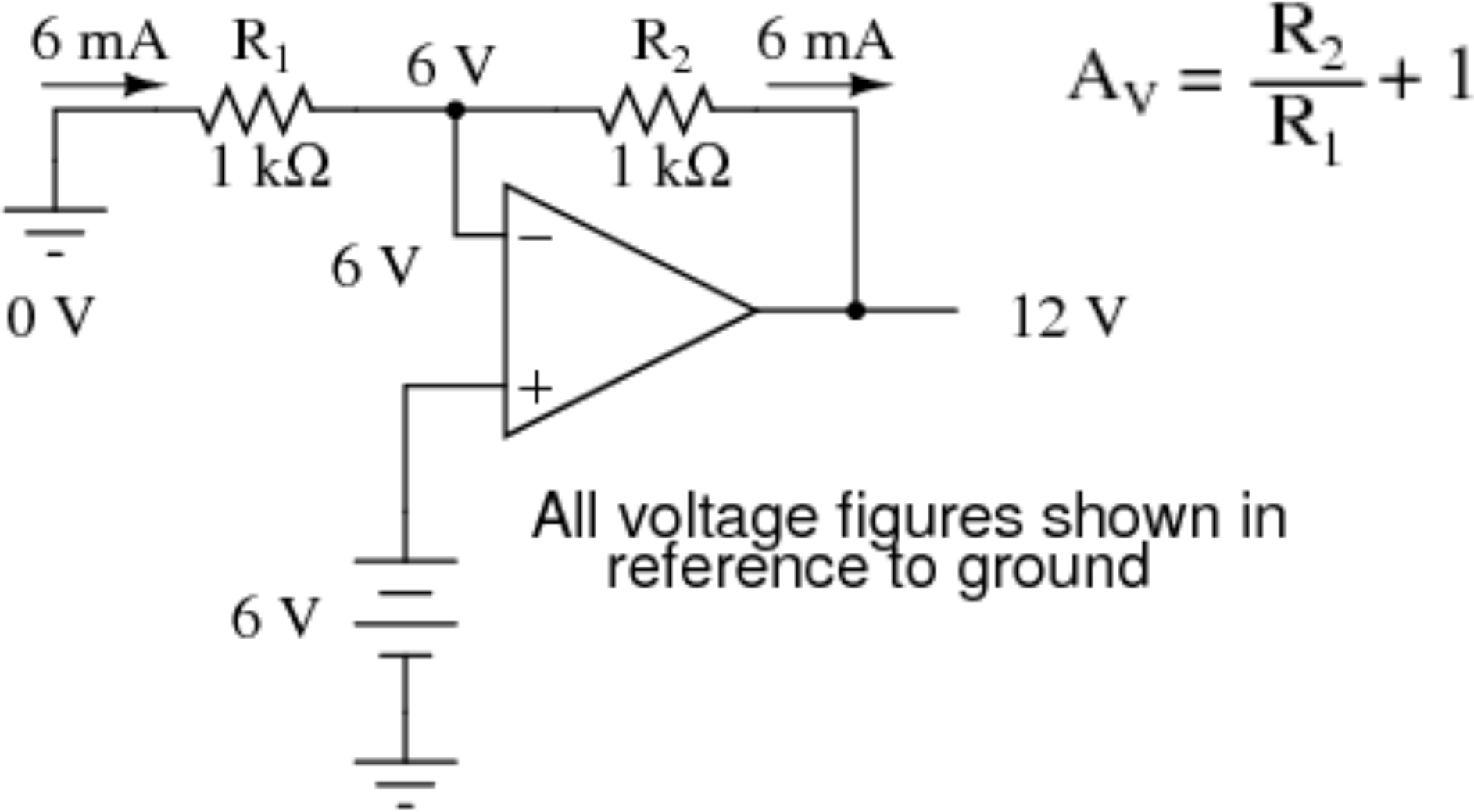
**We can place a voltage divider in the negative feedback loop to control the gain of the circuit (non-inverting amplifier)**

*The effects of divided negative feedback*



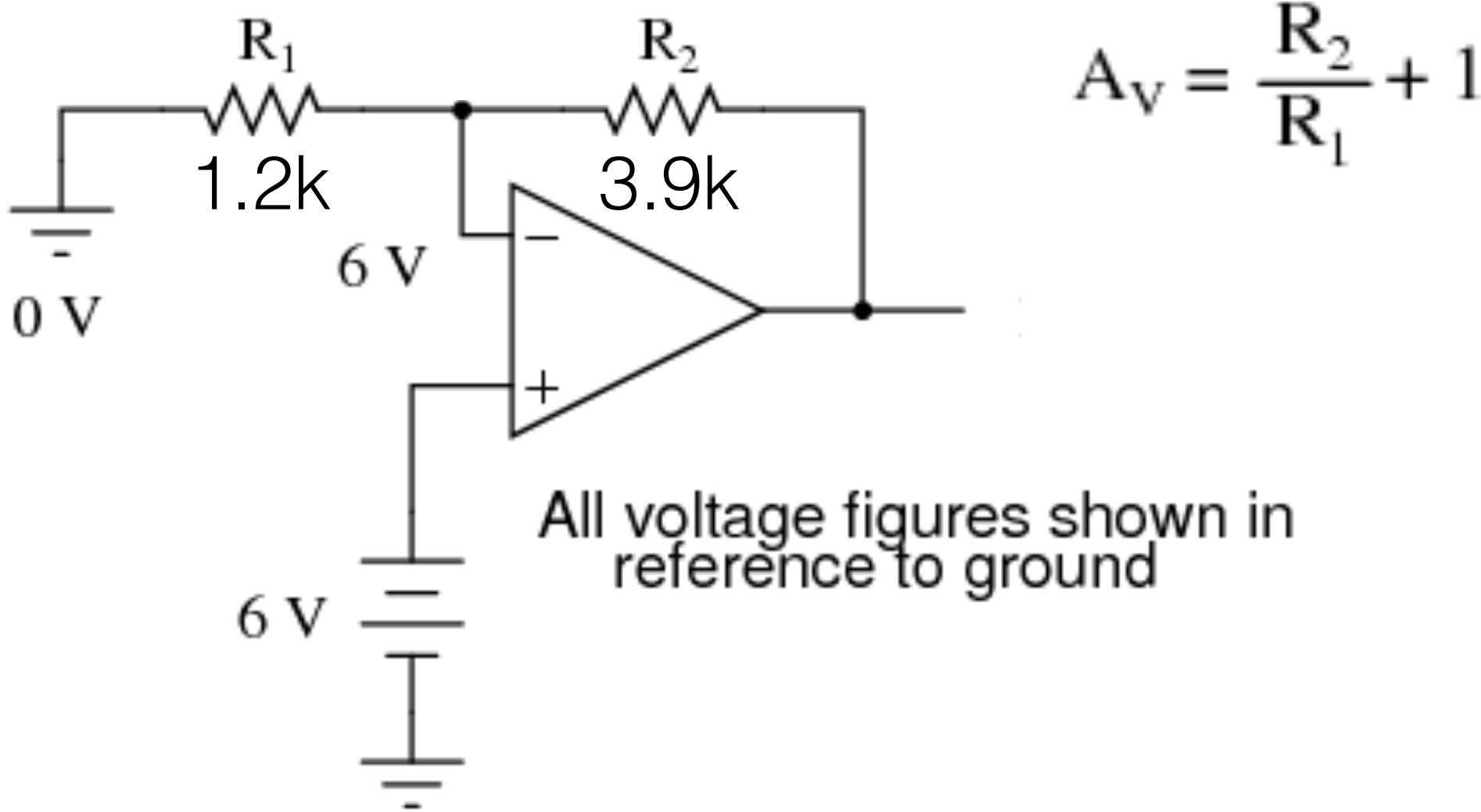
# Activity: What is the gain of this circuit? What is the output?

*The effects of divided negative feedback*



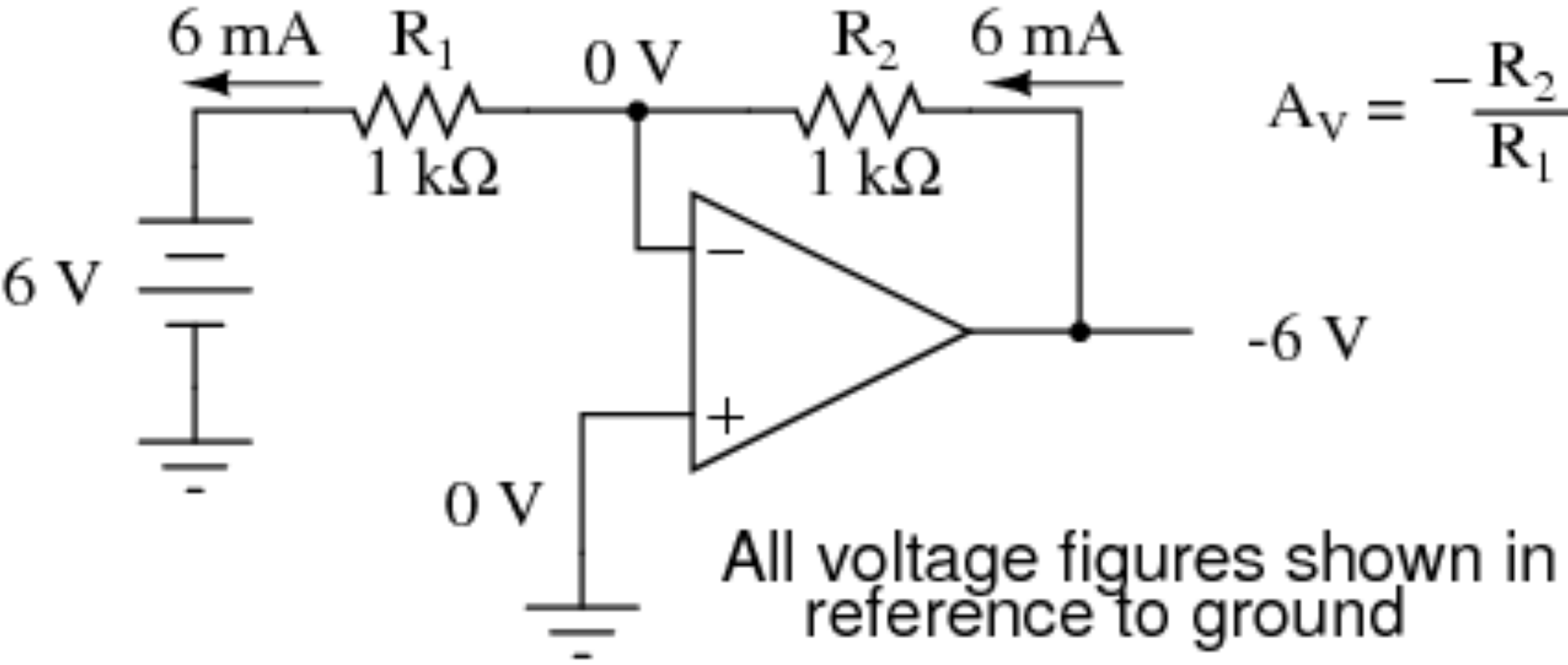
# By changing where the input is, we can create an inverting amplifier



All voltage figures shown in reference to ground


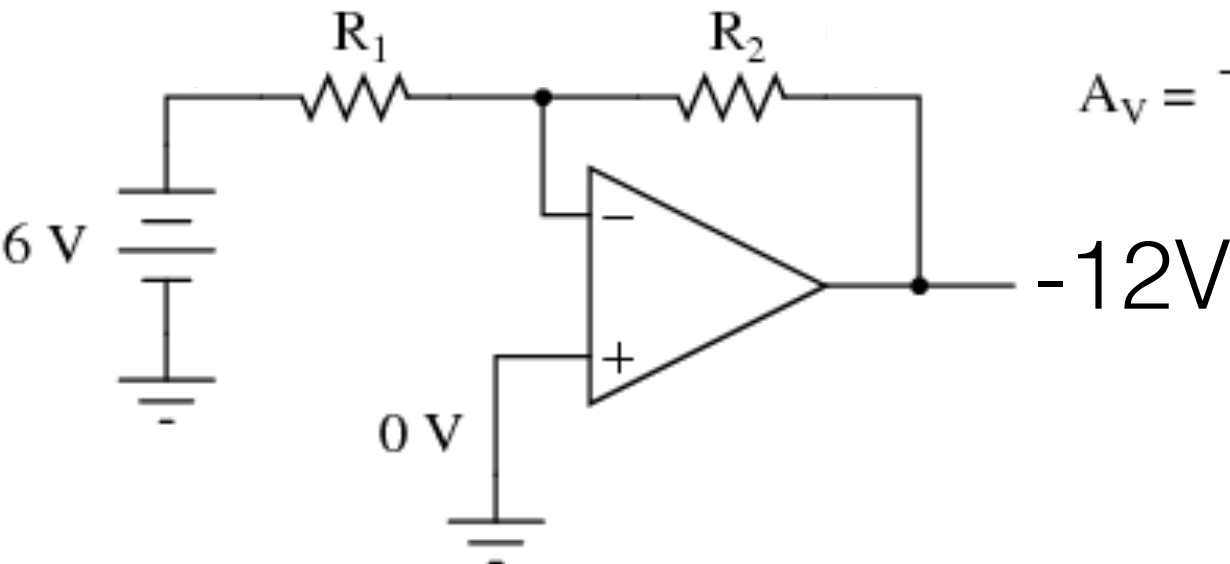
# Activity: What are valid combinations of standard value resistors for R1,R2?




$$A_V = -\frac{R_2}{R_1}$$


Standard Resistor Values ( $\pm 5\%$ )						
1.0	10	100	1.0K	10K	100K	1.0M
1.1	11	110	1.1K	11K	110K	1.1M
1.2	12	120	1.2K	12K	120K	1.2M
1.3	13	130	1.3K	13K	130K	1.3M
1.5	15	150	1.5K	15K	150K	1.5M
1.6	16	160	1.6K	16K	160K	1.6M
1.8	18	180	1.8K	18K	180K	1.8M
2.0	20	200	2.0K	20K	200K	2.0M
2.2	22	220	2.2K	22K	220K	2.2M
2.4	24	240	2.4K	24K	240K	2.4M
2.7	27	270	2.7K	27K	270K	2.7M
3.0	30	300	3.0K	30K	300K	3.0M
3.3	33	330	3.3K	33K	330K	3.3M
3.6	36	360	3.6K	36K	360K	3.6M
3.9	39	390	3.9K	39K	390K	3.9M
4.3	43	430	4.3K	43K	430K	4.3M
4.7	47	470	4.7K	47K	470K	4.7M
5.1	51	510	5.1K	51K	510K	5.1M
5.6	56	560	5.6K	56K	560K	5.6M
6.2	62	620	6.2K	62K	620K	6.2M
6.8	68	680	6.8K	68K	680K	6.8M
7.5	75	750	7.5K	75K	750K	7.5M
8.2	82	820	8.2K	82K	820K	8.2M
9.1	91	910	9.1K	91K	910K	9.1M

We can also use positive feedback, what happens if we ground the inverting input?



*Positive feedback*

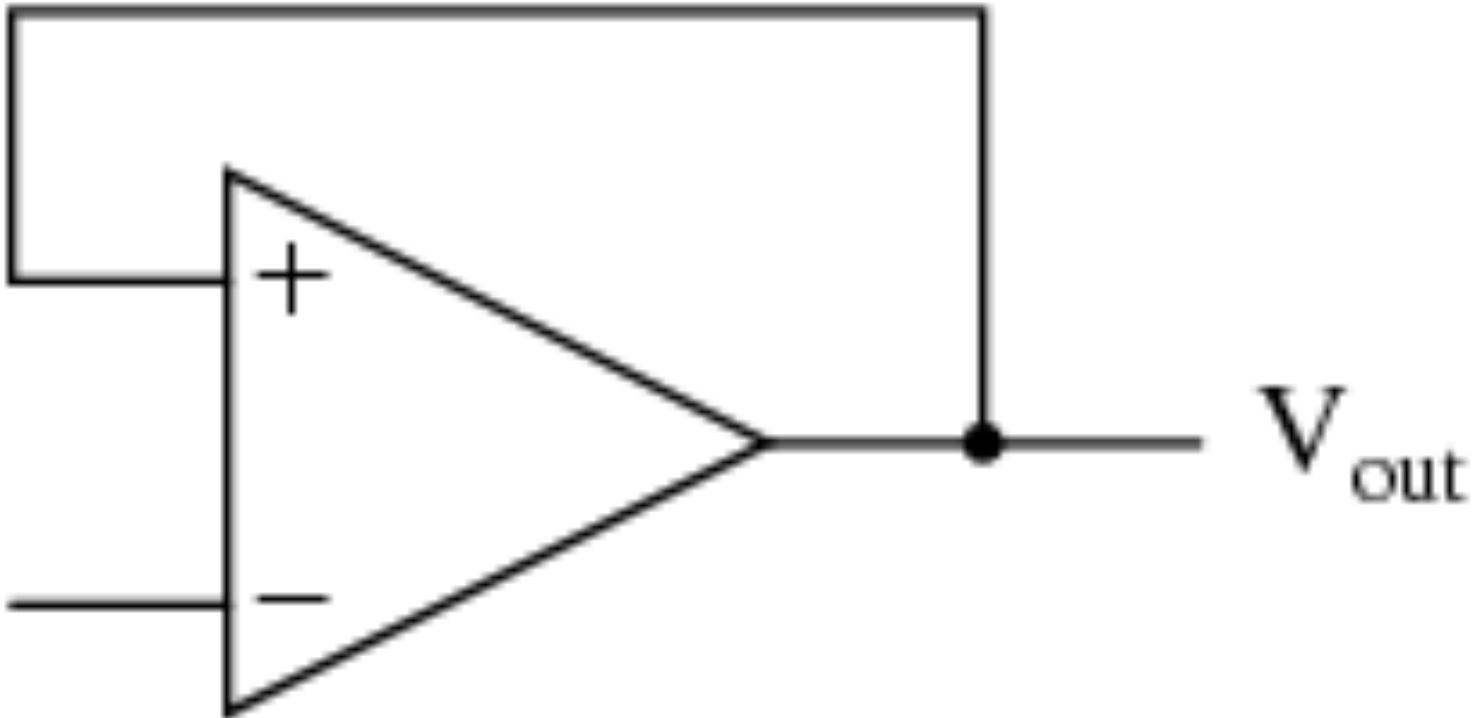

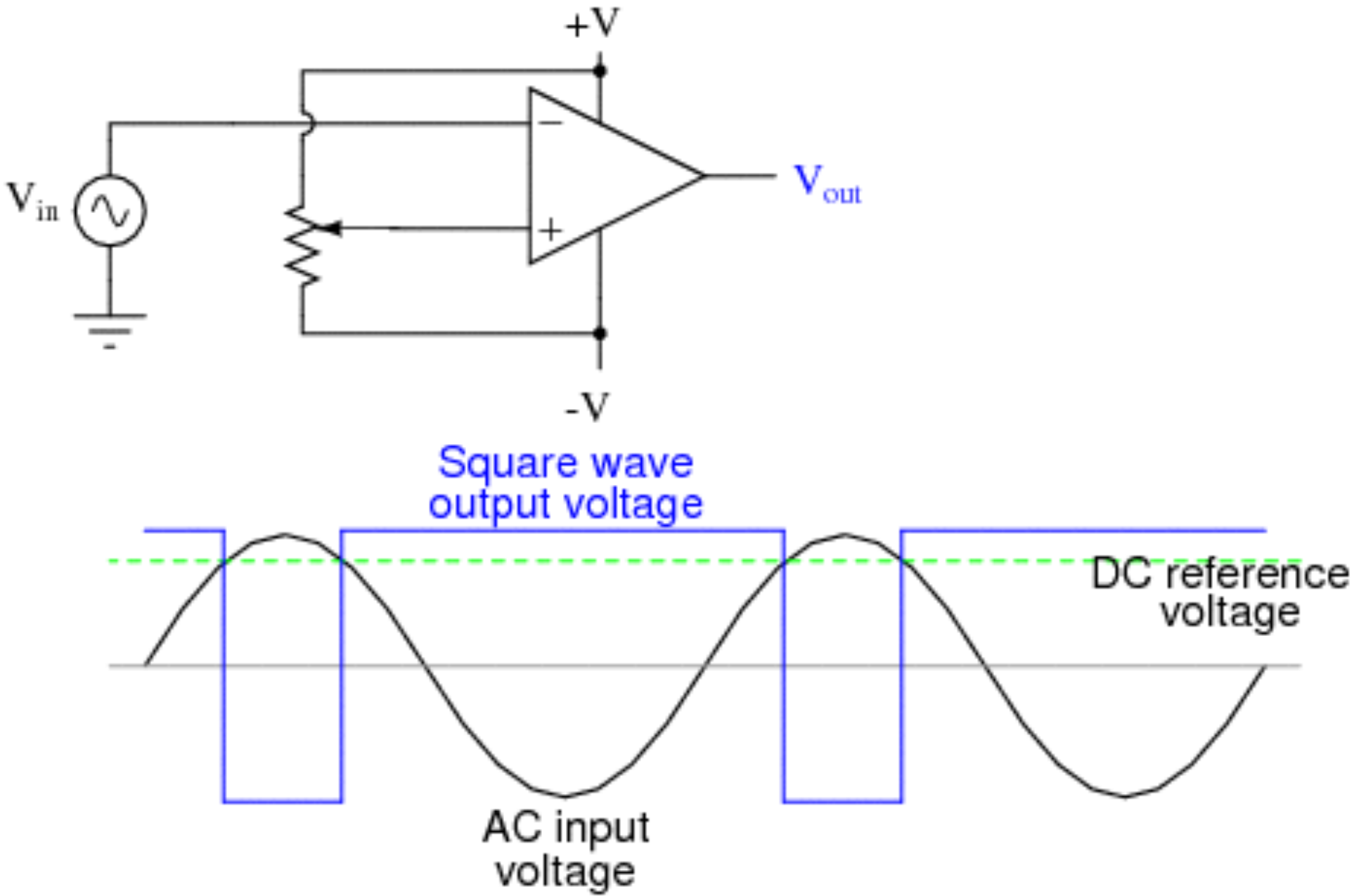
# Remember using a comparator to square a waveform?



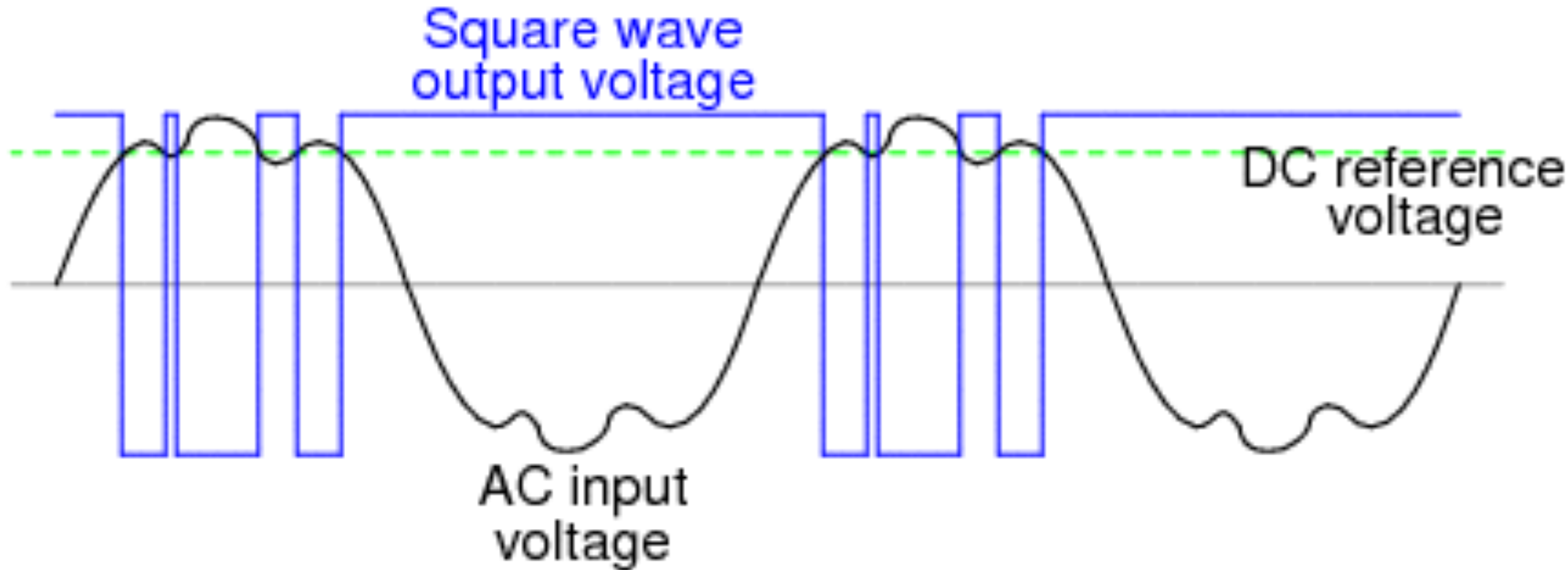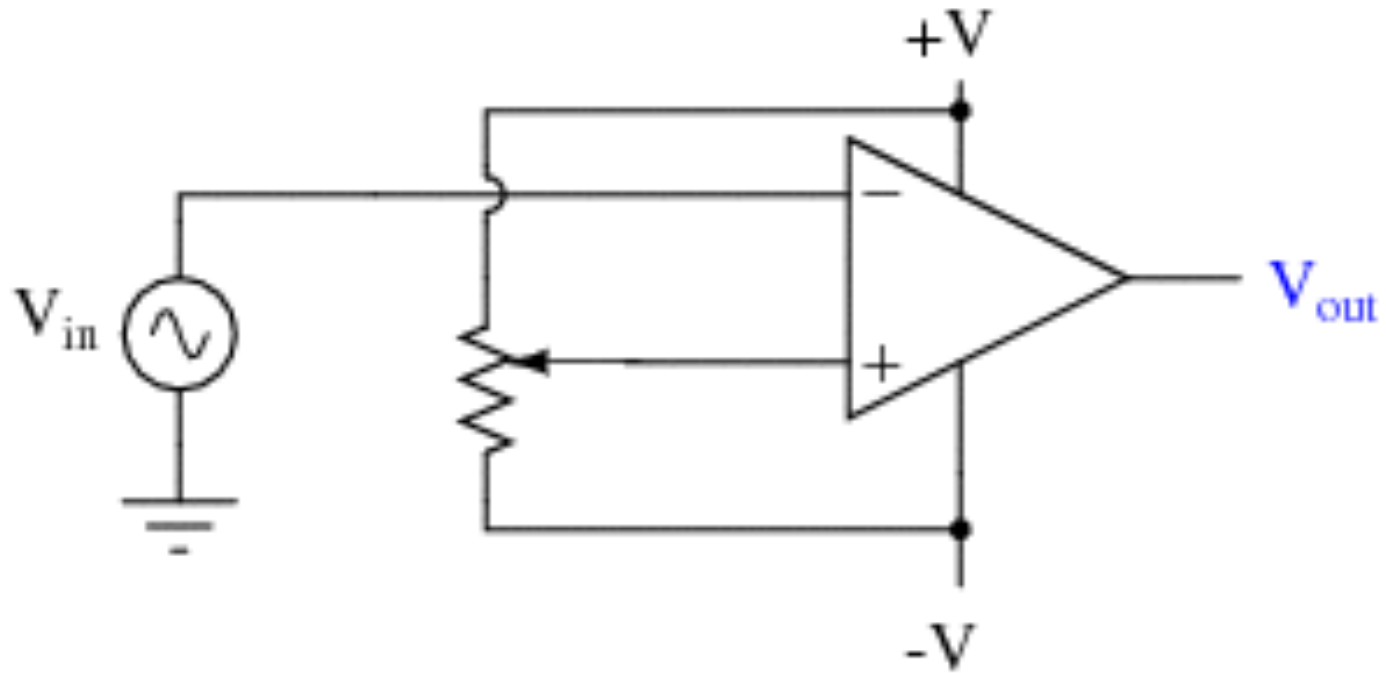
# What if there is some noise on the input waveform?


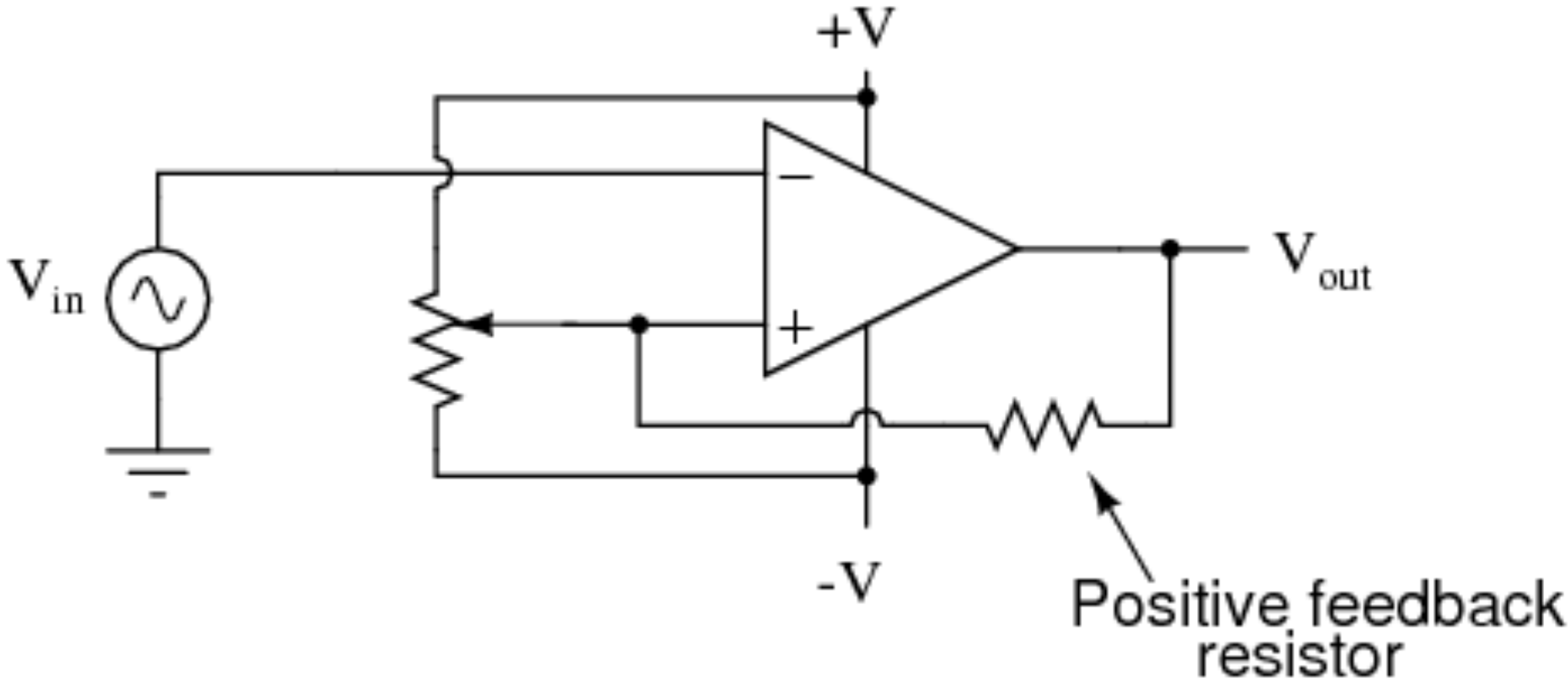
# Adding some positive feedback imposes hysteresis on the circuit



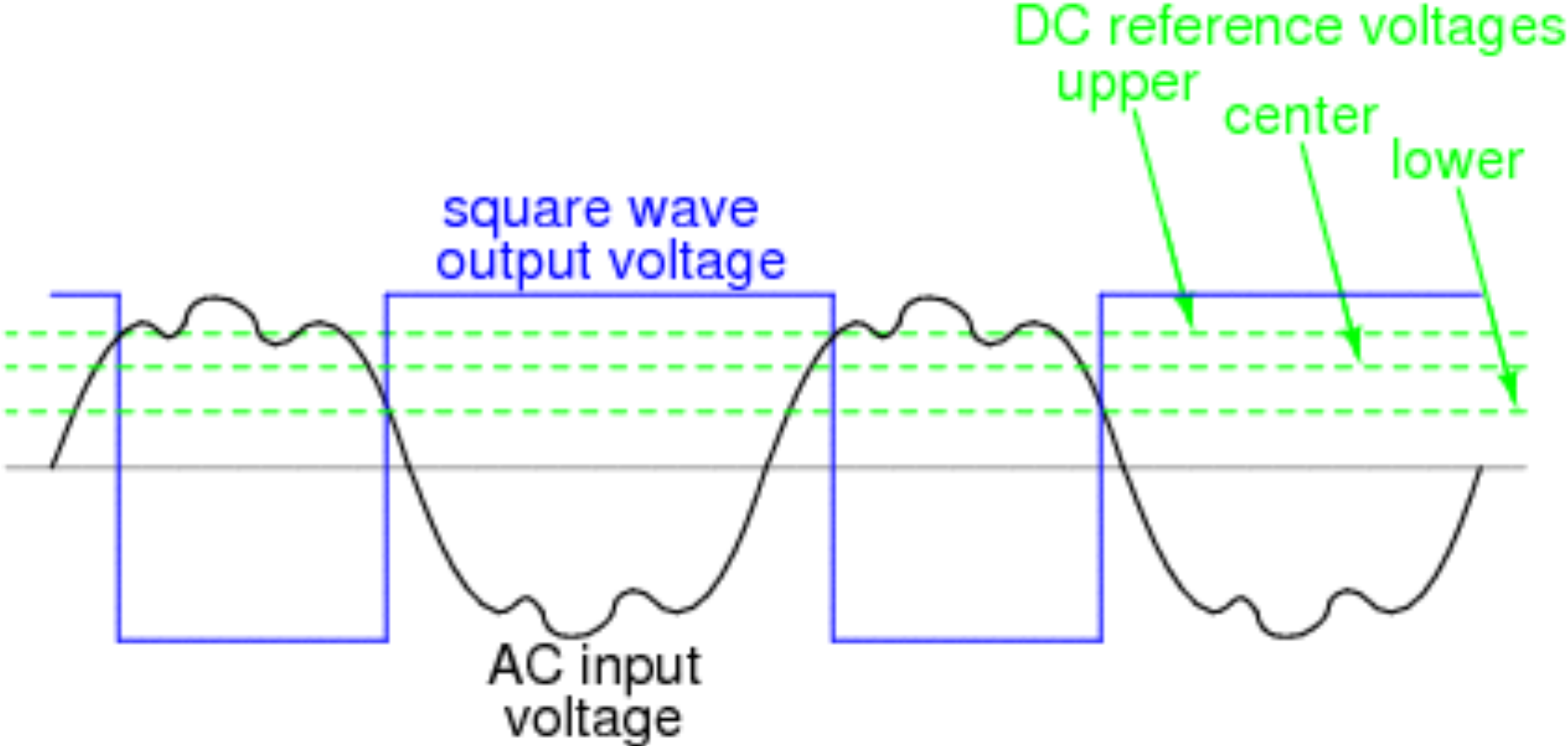
# This cleans the waveform up dramatically






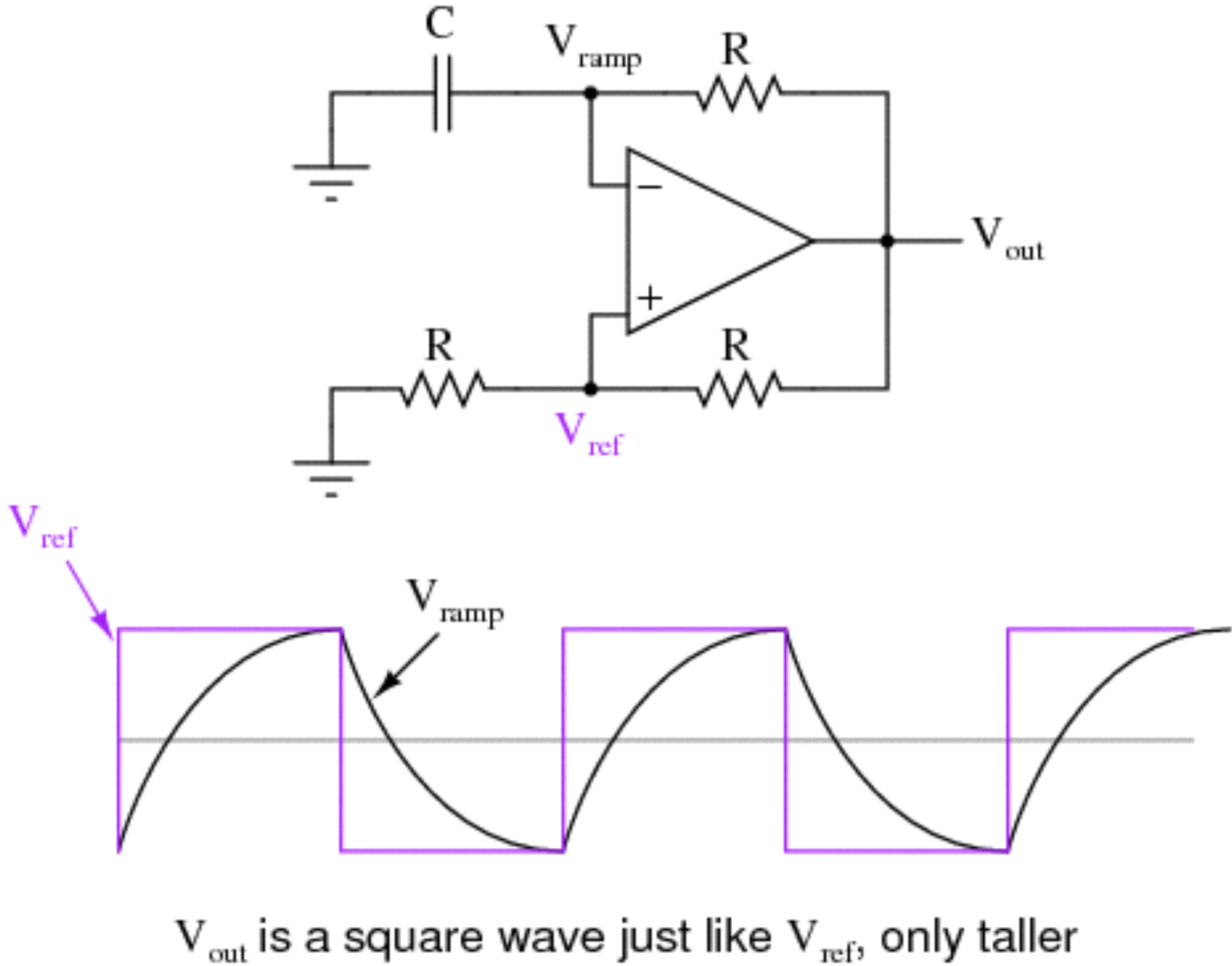
# We can even create an oscillator with positive feedback


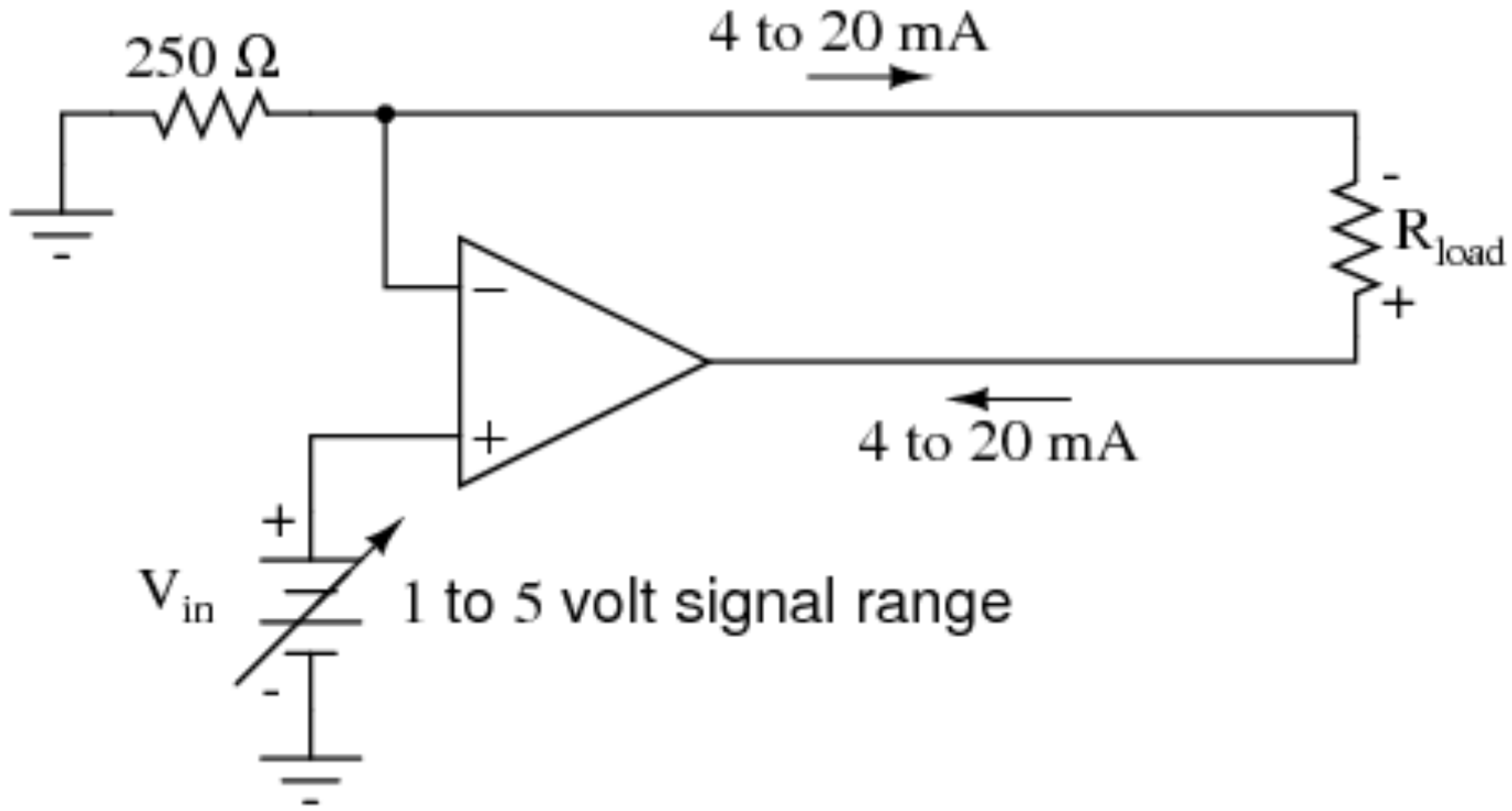
# We can make voltage to current converters with op-amps for long distance signaling


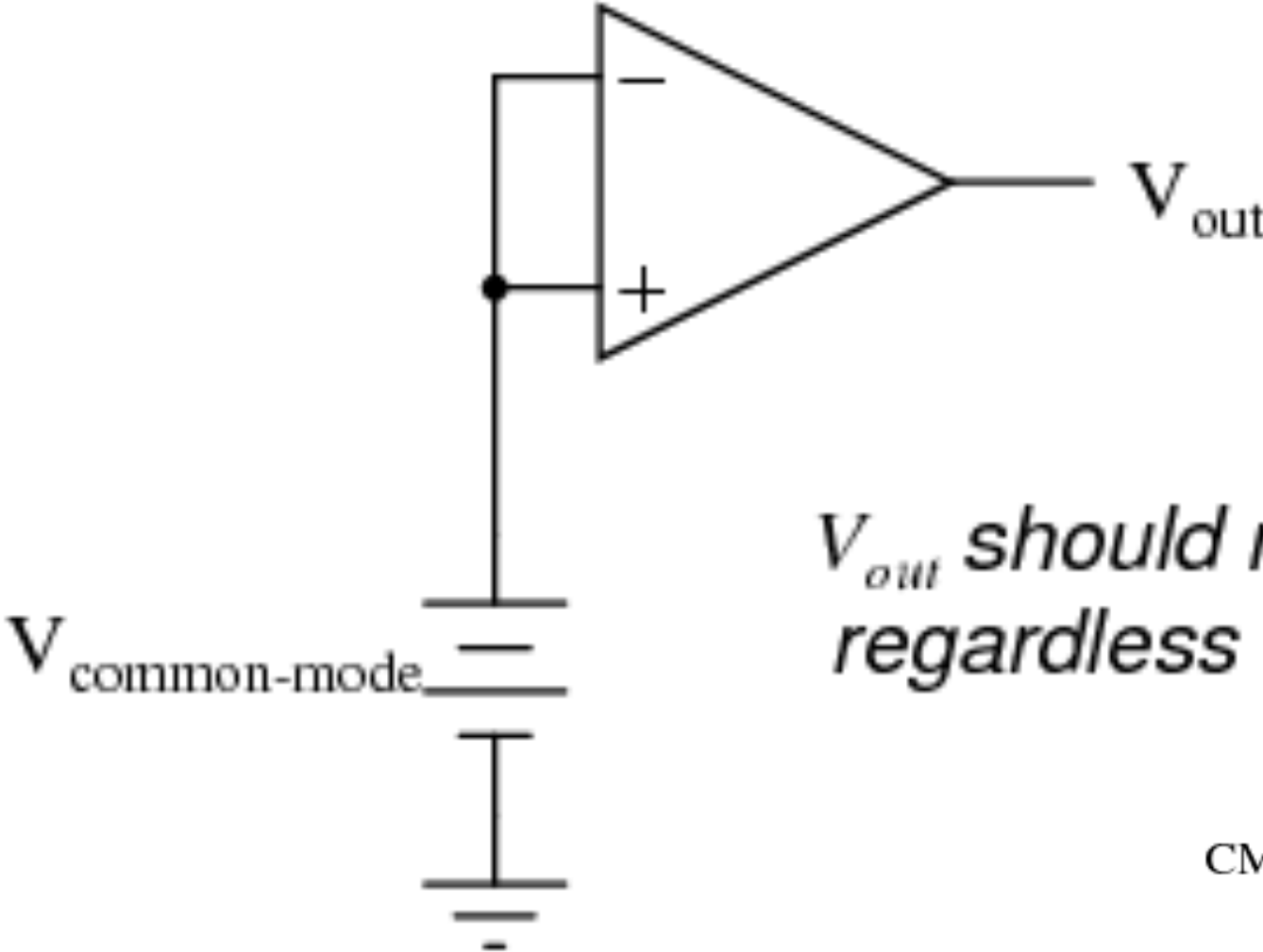
# Common mode rejection is a big spec to watch out for!



*$V_{\text{out}}$  should remain the same regardless of  $V_{\text{common-mode}}$*

$$\text{CMRR} = \frac{\text{Differential } A_v}{\text{Common-mode } A_v}$$


$$A_v = \frac{\text{Change in } V_{\text{out}}}{\text{Change in } V_{\text{in}}}$$

*... if change in  $V_{\text{out}} = 0$  ...*



$$\frac{0}{\text{Change in } V_{\text{in}}} = 0$$

$$A_v = 0$$
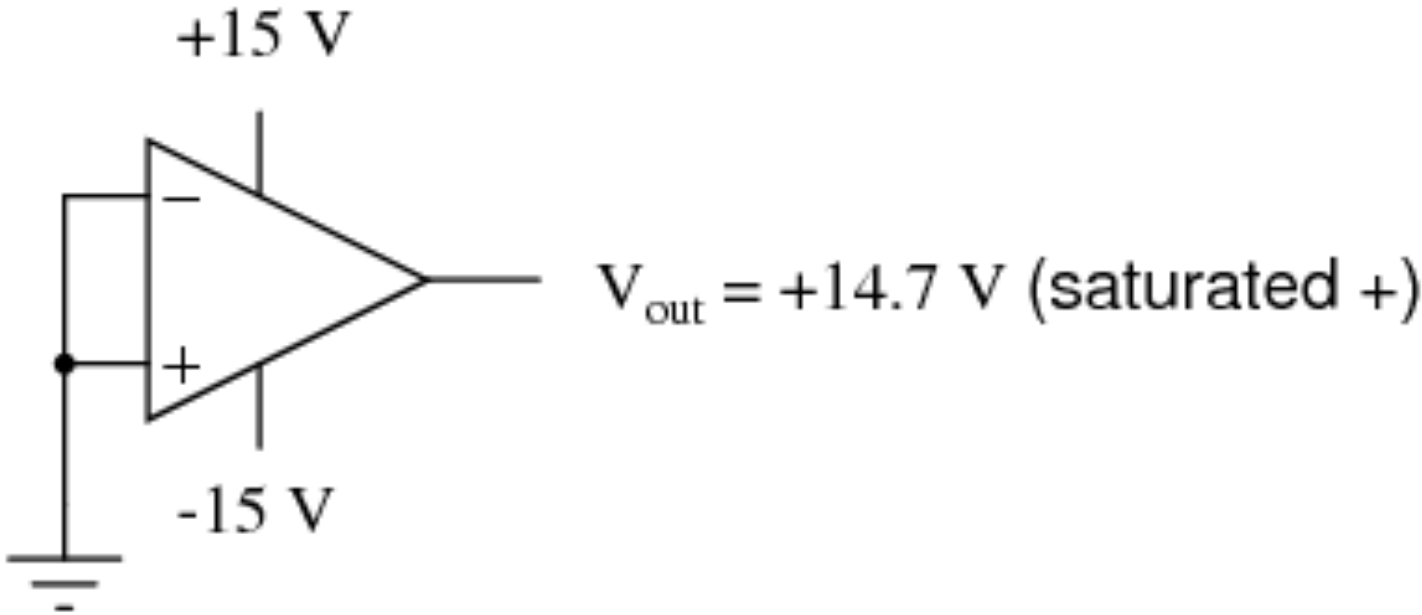
# Input offset voltage is another non-ideal characteristic of real op-amps



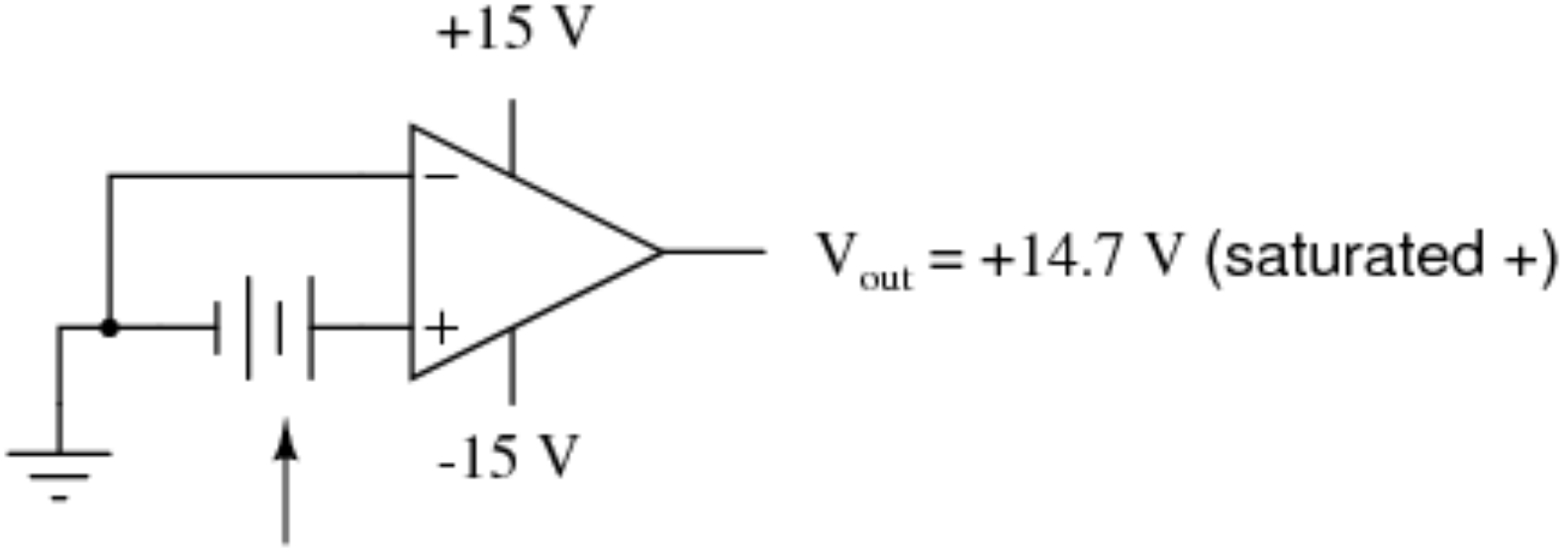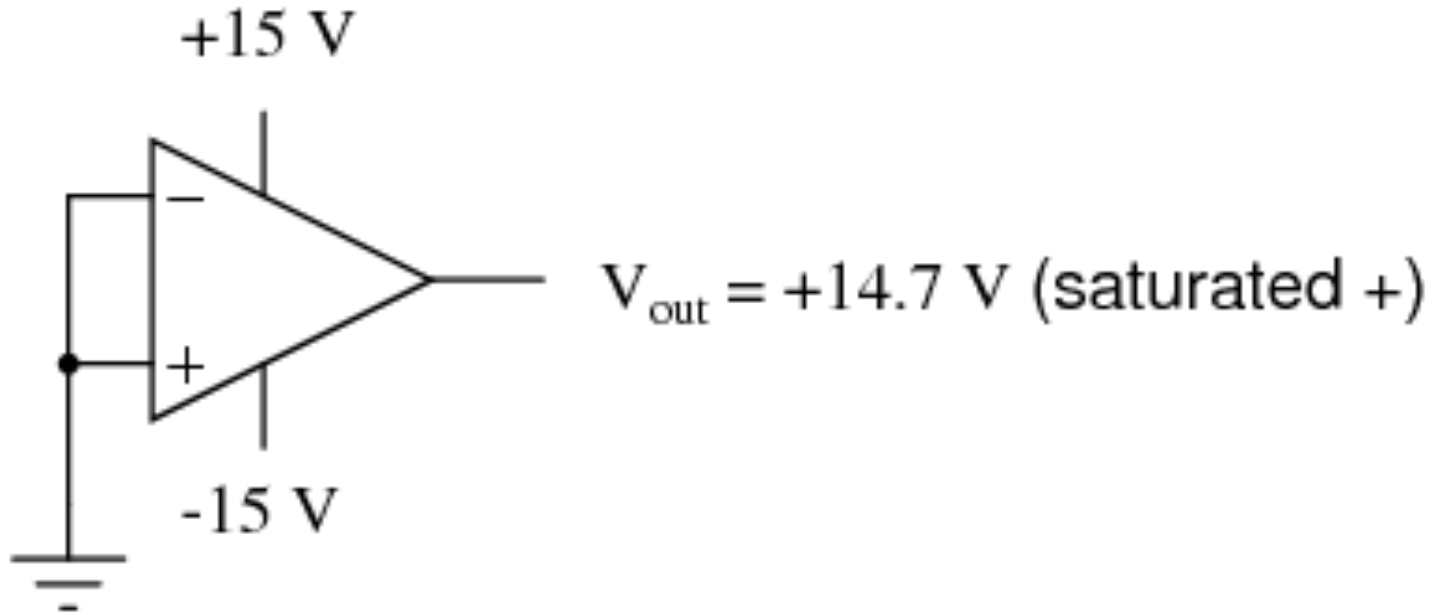
# Input offset voltage is another non-ideal characteristic of real op-amps



Input offset voltage  
*(internal to the real op-amp,  
external to this ideal op-amp)*

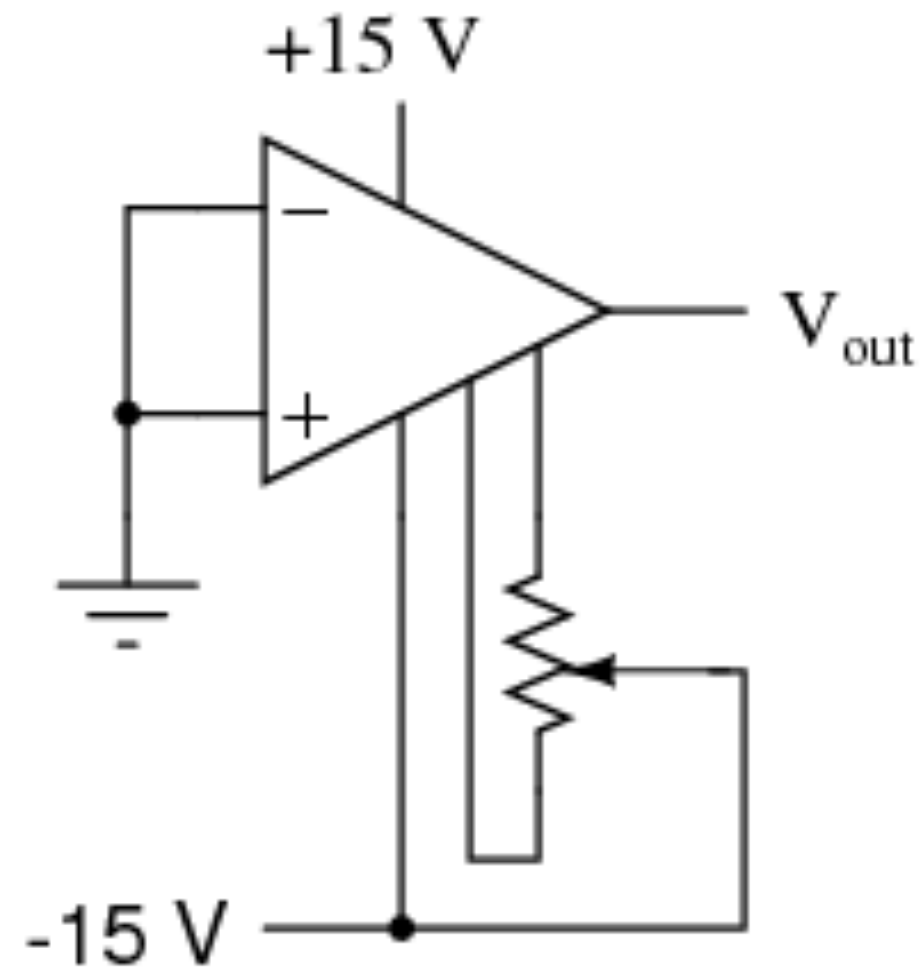
You can use a potentiometer to null the offset if necessary




*Potentiometer adjusted so that  $V_{out} = 0$  volts with inputs shorted together*


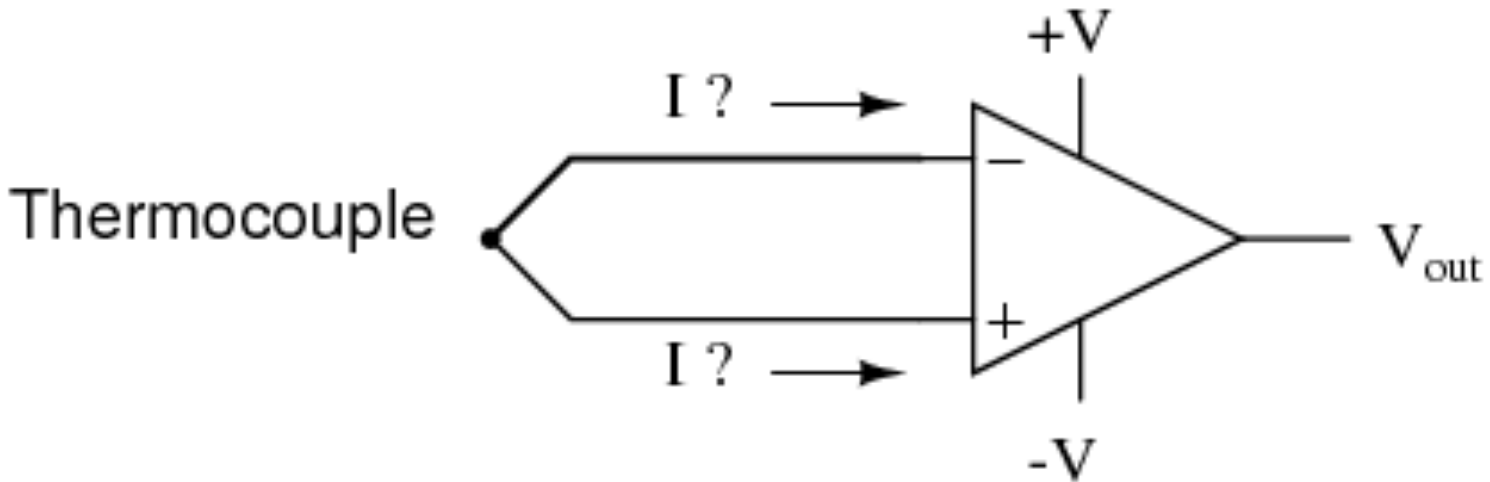
# Input bias currents need a ground path and can be a frustrating problem to realize




*This comparator circuit **won't** work*

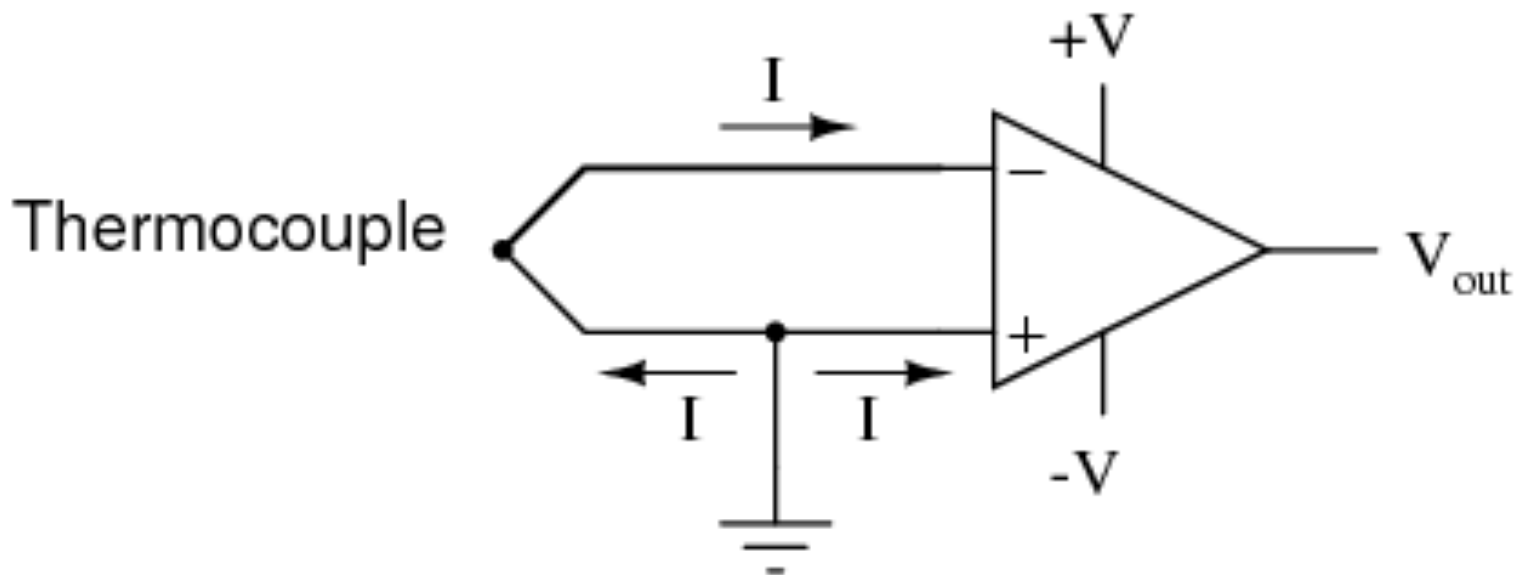

*This comparator circuit **will** work*
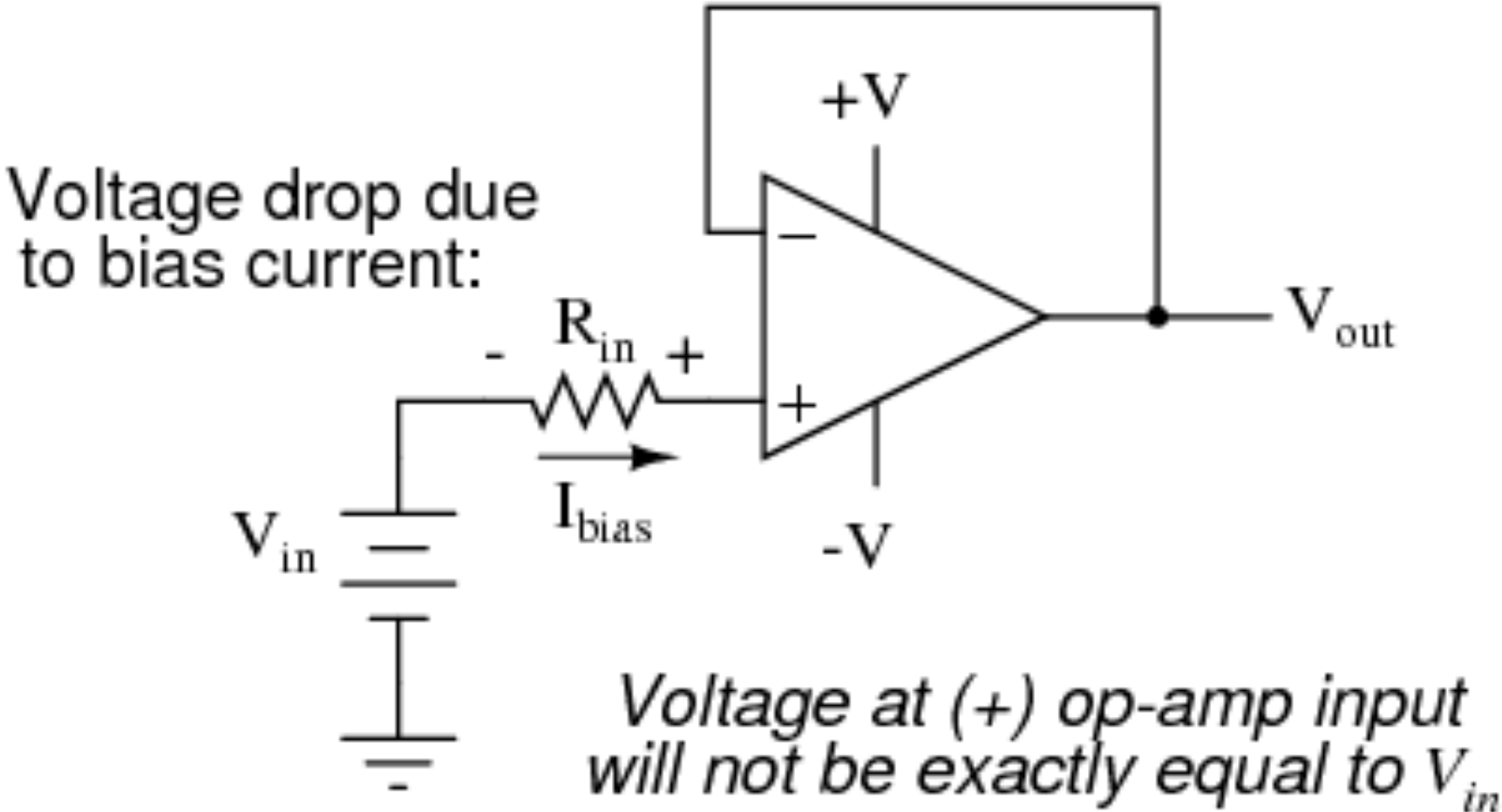
# They can also cause voltage drops that you don't expect



Like any semiconductor, there is a temperature drift



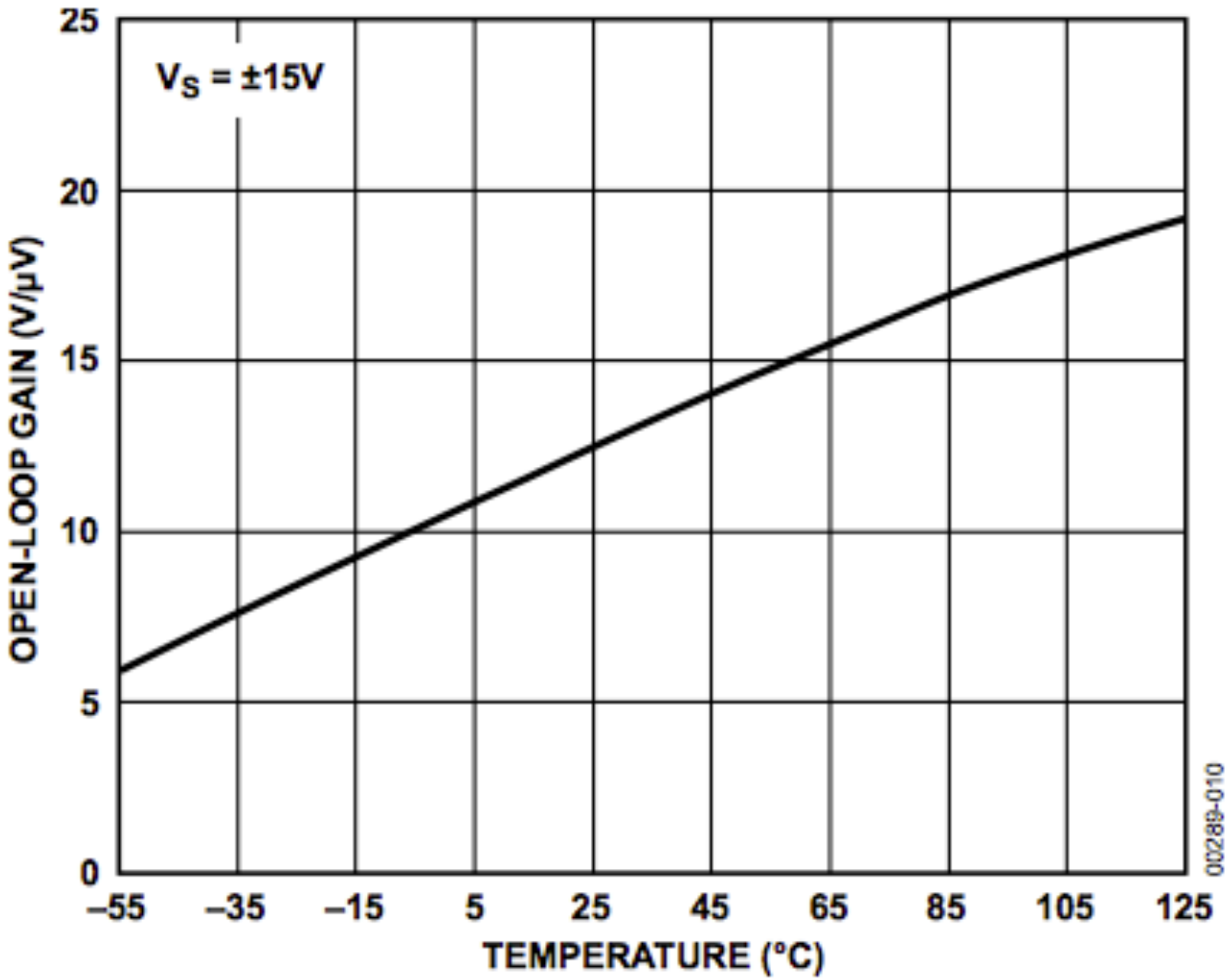


Figure 10. Open-Loop Gain vs. Temperature
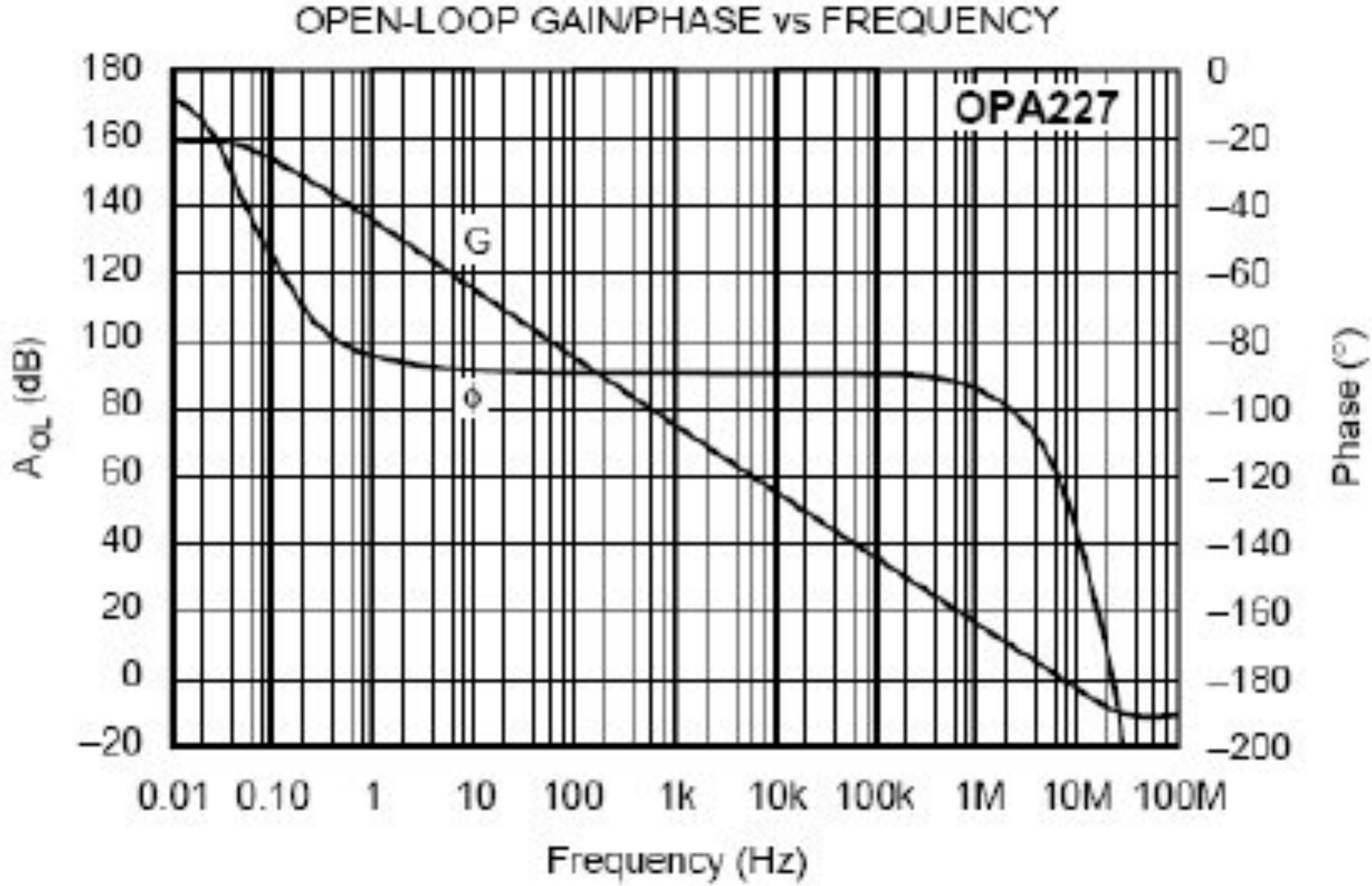
# Beware of the frequency response as well


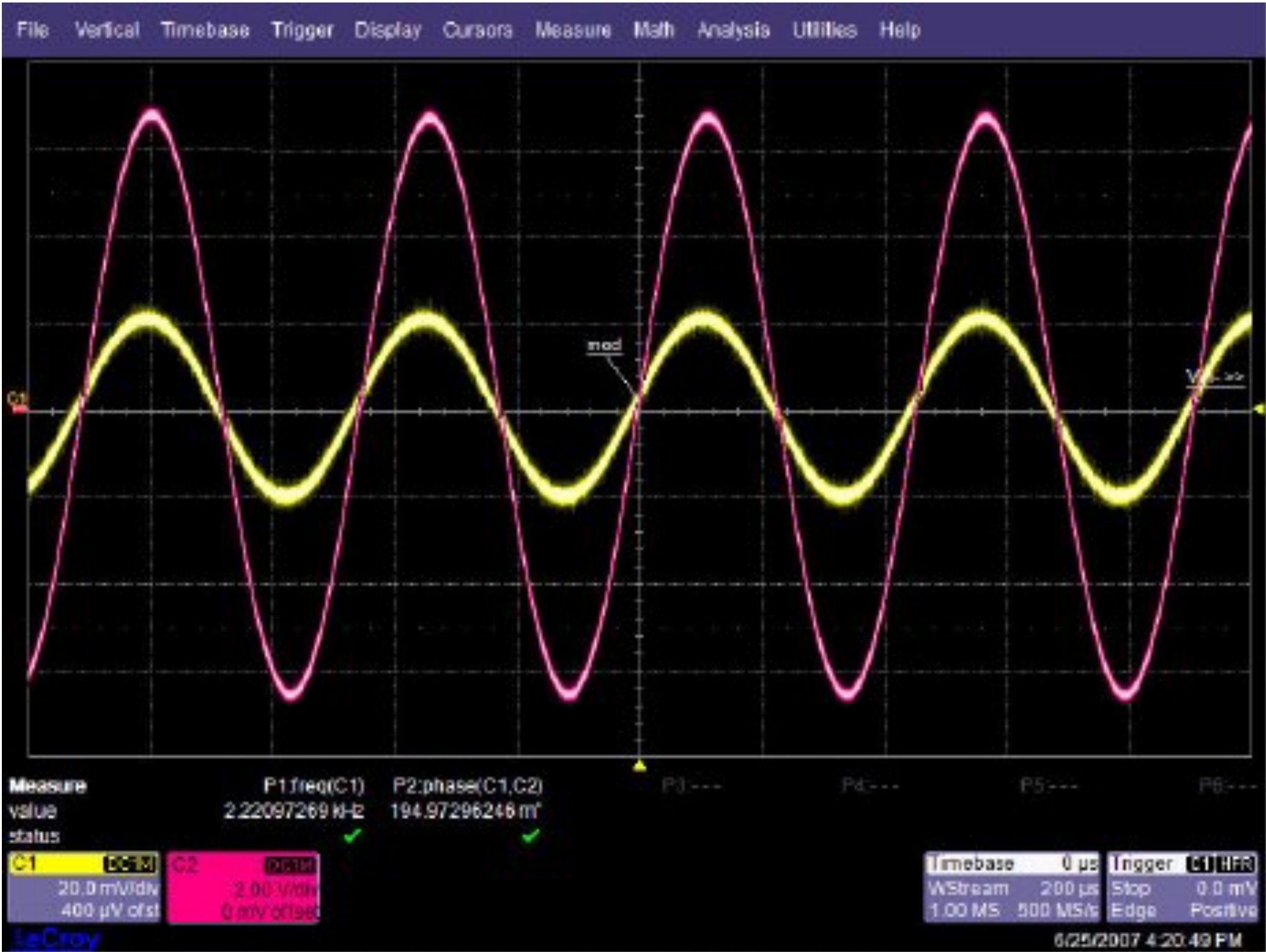
# Beware of the frequency response as well





# Beware of the frequency response as well



# Beware of the frequency response as well





**Assignment: Projects - it's time to start really cranking on them**

**Due : 10/25**